
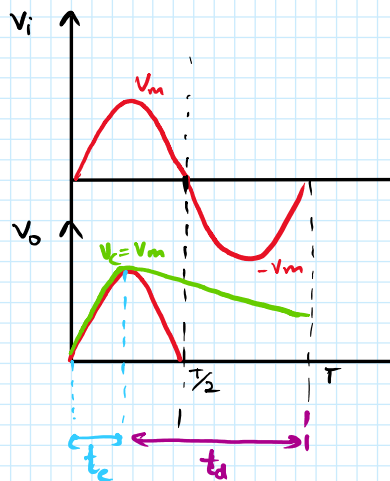


3. Parallel Capacitor Filter - HWR & FWR, Zener Diode Regulator

18 October 2023 14:43

SCHUNT / PARALLEL CAPACITOR FILTER

HWR



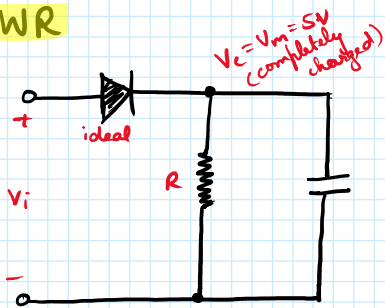


$$\gamma = \frac{V'_{rms}}{V_{dc}} \quad \gamma = \frac{1}{2\sqrt{3}fCR_L}$$

$$V_{dc} = V_m - \frac{I_{dc}}{2fC} \quad V'_{rms} = \frac{I_{dc}}{2\sqrt{3}fC}$$

$$t_c + t_d = T$$

CENTRE TAP FWR / BRIDGE FWR

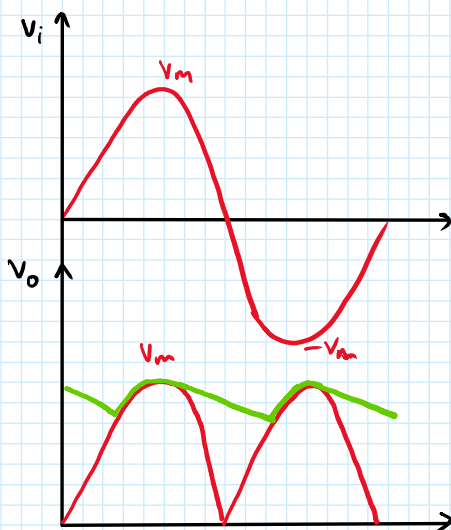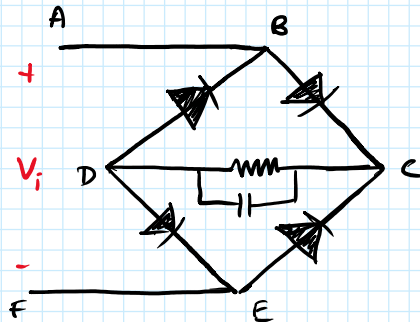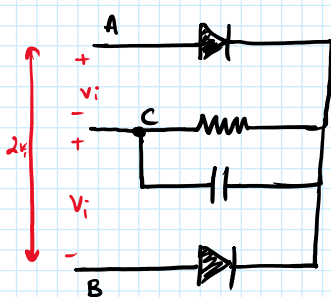

$$\gamma = \frac{V'_{rms}}{V_{dc}}$$

$$V'_{rms} = \frac{I_{dc}}{4\sqrt{3}fC}$$

$$\gamma = \frac{1}{4\sqrt{3}fCR_L}$$

$$V_{dc} = V_m - \frac{I_{dc}}{4fC}$$

PROBLEMS

- ① A full wave rectifier with C filter is supplying a load of 500Ω . If the ripple factor should not exceed 10%, find the value of capacitor required. Assume input AC signal frequency is 50 Hz. What is the new value of γ if capacitor of $500\mu F$ is connected across the load?

Soln. $\gamma = \frac{1}{4\sqrt{3} f C R_L}$

$$C = \frac{1}{4\sqrt{3} f \gamma R_L}$$

$$= \frac{1}{4\sqrt{3} \times 50 \times 0.1 \times 500} = 57.73 \mu F$$

If $C = 500 \mu F$,

$$\gamma = \frac{1}{4\sqrt{3} f C R_L} = \frac{1}{4\sqrt{3} \times 50 \times 500 \times 500}$$

max load current $\rightarrow I_m$
load current $\rightarrow I_{dc}$
 I_{dc}

- ② In a full wave rectifier with C filter the output DC voltage is 10V and load current is 10mA. Calculate the value of capacitance required such that the output DC voltage will have ripple ≤ 0.001 . Find V_m .

Soln. $R_L = \frac{V_{dc}}{I_{dc}} = \frac{10}{10m} = 1k\Omega$

Assume frequency of input AC signal


$$\gamma = \frac{1}{4\sqrt{3} f C R_L}$$

$$C = \frac{1}{4\sqrt{3} f \gamma R_L} = \frac{1}{4\sqrt{3} \times 50 \times 0.001 \times 1 \times 10^3} = 2886 \mu F$$


V_{dc}

ZENER DIODE REGULATOR



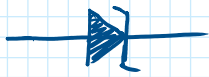


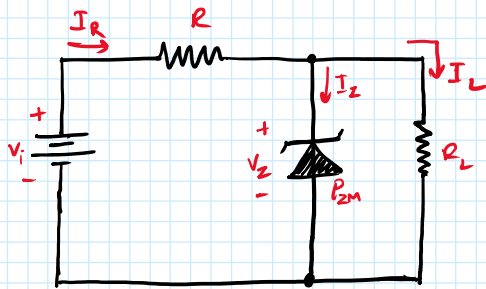Case ①: Fixed V_i (supply voltage) and fixed R_L (load)



Step ①: Remove the diode to determine state of the diode, by calculating voltage across the resulting open circuit.
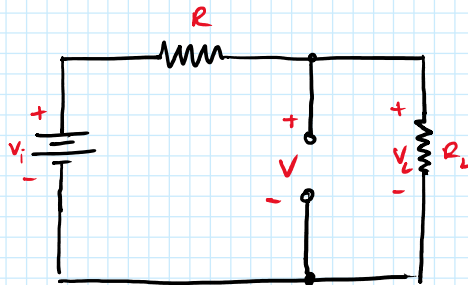
$$V = V_L = \frac{R_L \cdot V_i}{R + R_L}$$



Step ②: Substitute the appropriate equivalent circuit and solve for unknowns.

If $V < V_Z \longrightarrow$ Diode is OFF, then circuit equivalent is substitute

If $V \geq V_Z \longrightarrow$ Diode is ON, appropriate equivalence model is substituted
Once the diode is ON, it will "lock in" its value of V_Z

By KCL,

$$\text{Total current } I_R = I_Z + I_L$$

$$I_L = \frac{V_L}{R_L}$$

$$I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$

$$P_Z = V_Z I_Z$$

\rightarrow Power dissipated by Zener diode