
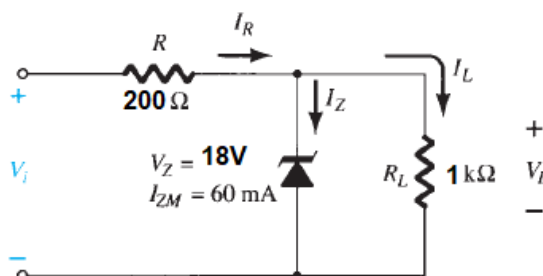


May 2022: END SEMESTER ASSESSMENT- B.TECH. I/II SEMESTER
UE20EC101 – Electronic Principles and Devices

Time: 180 mins		Answer All Questions	Max Marks: 100
1.	a	With a neat circuit diagram Explain Forward and Reverse Characteristics of a semiconductor Diode. Discuss the effect of Temperature on V-I Characteristics.	8 M
	b	Use Second approximation for a diode to determine the unknown values for the following. (i) Determine I_D and V_o for the circuit shown in the Figure below. (ii) Determine I and V_o for the circuit shown in the Figure below	6M
	c	Using Shockley's equation, Find the diode current I_d for a silicon Diode if the applied voltage $V_D=0.71$ V if the Reverse Saturation is 4×10^{-12} A at a temp of 30° C. Consider ($\eta=1$). Find the new I_d if the temperature is increased by 20° C.assuming same V_D .	6M
2.	a	Calculate the RMS value of the ripple voltage for the FWR if a $100\mu\text{F}$ Capacitor is connected to a load drawing 50mA of current. What is the dc voltage at the output if the peak rectified output voltage is 30V and frequency is 50Hz? Also find the ripple factor.	7M
	b	With a neat diagram, explain the working principle of Full wave Rectifier with Centre tapped Transformer and derive the expression for V_{dc} and V_{rms}	6M
	c	Determine the range of values of V_i that will maintain the Zener diode in the “on” state for the following Circuit.	7M
3.	a	Explain the following Logical gates and realize using any Universal Gates. (i) NOR (ii) XOR (iii) AND (iv) NOT	8 M

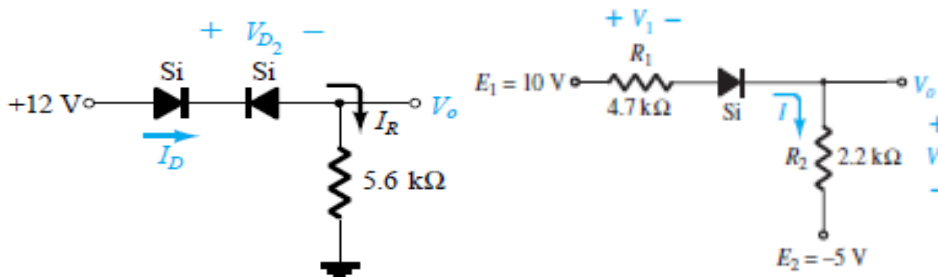

	b	With Characteristic Table and a neat circuit Diagram using ONLY NAND Gates, explain JK Flip flop.	6 M
	c	Define shift register. Draw the circuit diagram for 4-bit shift register and explain with example.	6 M
4.	a	With a neat diagram, explain the Input and output V-I characteristics of PNP Common Base BJT. Find the value of α and I_B , if $I_E = 1.32\text{mA}$ and $I_C = 1.11\text{mA}$.	7M
	b	With a neat block diagram, explain Communication System.	7M
	c	What are the Principles of Cellular Communication? Explain	6 M
5	a	Give the Differences between Microprocessor and Microcontroller	8M
	b	Explain the Data Flow Model of ARM Processor with a neat diagram.	4 M
	c	With examples illustrate the usage of embedded systems for the following various Applications.	8 M