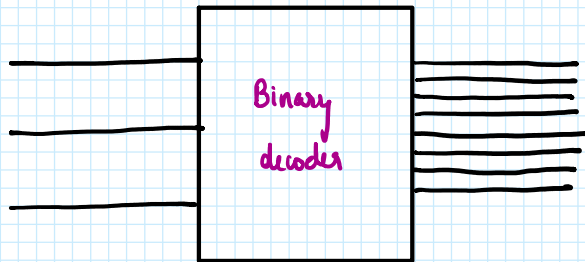


4. Combinational: Decoders, Encoders, Comparators

26 August 2024 08:54

DECODERS

n inputs $\rightarrow 2^n$ outputs : no select signal and no demarcation of control & data signal



Data signal itself is the control signal

ENCODERS

Opposite of decoders

2^n inputs $\rightarrow n$ outputs

8:3 \rightarrow Octal to binary


- At any given time, only one input line is at 1

Priority encoder

If more than one input line is high, the higher input is given priority to get output.

$D_2 D_1$	$D_2 D_1$	01	01	11	10
00	X	1	1		
01	1	1	1		
11	1	1	1		
10		1	1		

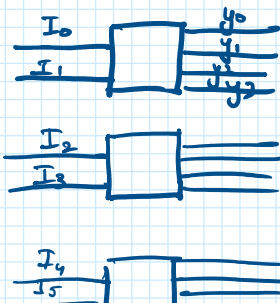Construct 4:16 line decoder with 5 2:4 line decoders with enable.





Let $A = A_3 A_2 A_1 A_0$
 $B = B_3 B_2 B_1 B_0$

$$\begin{array}{r}
 \begin{array}{cccc}
 & & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & & A_2 B_0 & A_1 B_0 & A_0 B_0 \\
 & A_2 B_1 & A_1 B_1 & A_0 B_1 & \\
 & A_2 B_2 & A_1 B_2 & A_0 B_2 & \\
 + & A_2 B_3 & A_1 B_3 & A_0 B_3 & \\
 \hline
 C_6 & C_5 & C_4 & C_3 & C_2 & C_1 & C_0
 \end{array}
 \end{array}$$

FOUR BIT ADDER SUBTRACTOR (w/ OVERFLOW DETECTION)

Let $A = A_3 A_2 A_1 A_0$

$B = B_3 B_2 B_1 B_0$

Can perform either $A+B$ or $A-B$ ($A+(-B)$)

$-B = 2$'s complement of $B = \bar{B} + 1$

TWOS COMPLEMENT NONSENSE

BCD ADDER (DECIMAL ADDER)