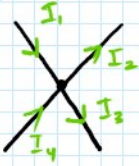


2. Kirchhoff's Laws, Types of Connections

07 February 2024 12:37

KIRCHHOFF'S CURRENT LAW (KCL)

At any particular junction, sum of all currents is zero



KIRCHHOFF'S VOLTAGE LAW (KVL)


Around every closed path in a network, sum of voltages is zero

Voltage drop \rightarrow negative

Voltage rise \rightarrow positive


EXAMPLE

Find the current through 8Ω resistor.

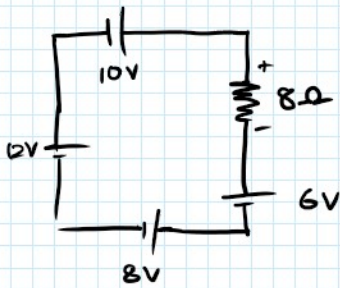

$$\begin{aligned} 10 - 8I - 6 + 8 + 12 &= 0 \\ -8I &= -8 \\ I &= \frac{-8}{-8} = 1A \end{aligned}$$

Find voltage V_{AB}

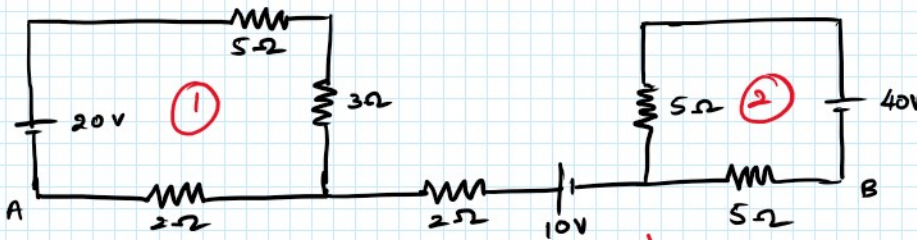

In ①,

$$20 - 5I_1 - 3I_1 - 2I_1 = 0$$

$$20 - 10I_1 = 0$$

$$10I_1 = 20$$

$$I_1 = 2A$$

Drop across $2\Omega = 4V$


In ②,

$$40 - 5I_2 - 5I_2 = 0$$

$$I_2 = \frac{40}{10}$$


$$I_2 = 4A$$

Drop across $5\Omega = 20V$

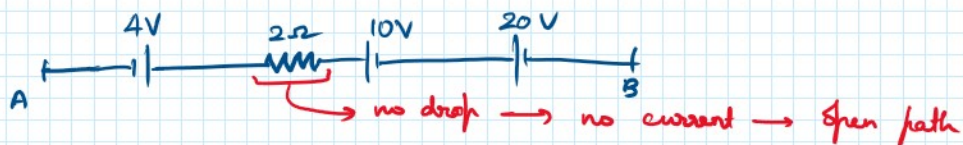

$$V_{AB} = 20 + 10 - 4 = \underline{\underline{26 \text{ V}}}$$

Find the current in the branch XY.

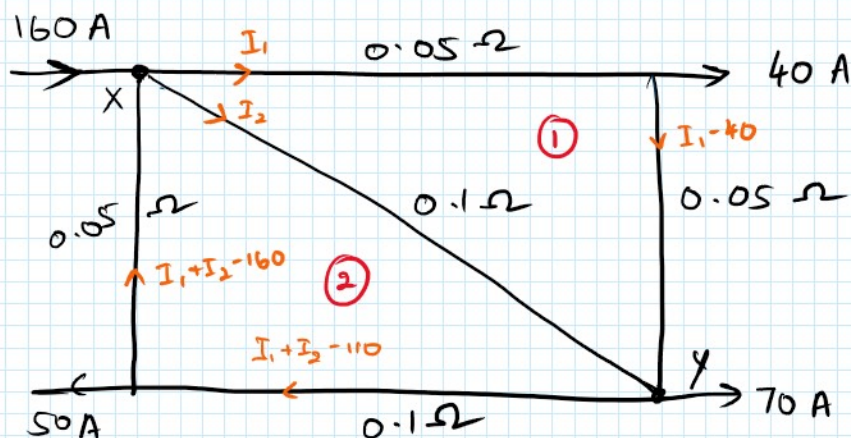

In ①,

$$-0.05I_1 - 0.05(I_1 - 40) + 0.1(I_2) = 0$$


$$0.1I_1 - 0.1I_2 = 2$$

In ②,


$$-0.1I_2$$

TYPES OF CONNECTION

① SERIES CONNECTION

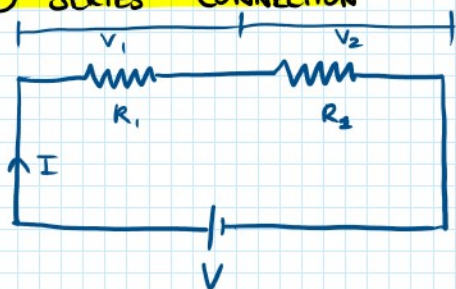

EXAMPLE

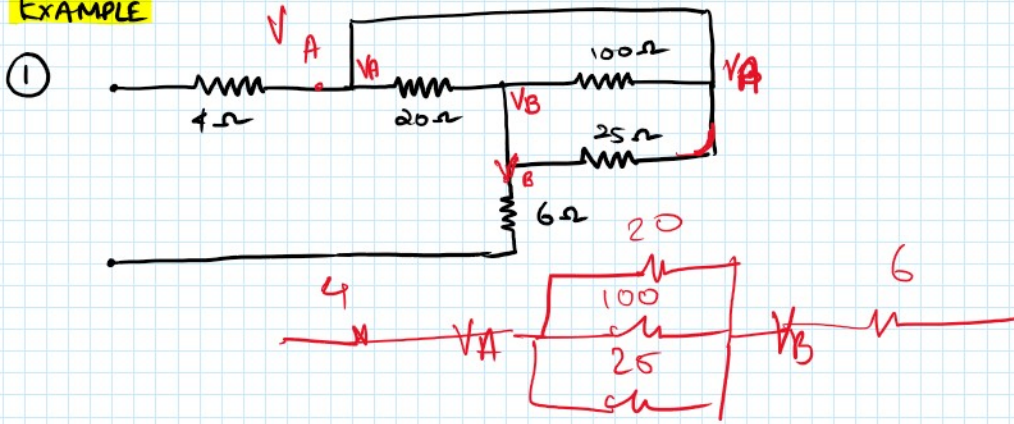

$$\frac{1}{20} + \frac{1}{100} + \frac{1}{25} = \frac{1}{R} \Rightarrow \frac{5+1+4}{100} = \frac{10}{100} = \frac{1}{10} = \frac{1}{R}$$

$$R = 10\Omega$$

