


4. Power Factor Improvement

15 March 2024 09:01

POWER FACTOR


- I^2R losses reduced
- Reactive power reduces
- Higher PF \rightarrow utilises higher capacity of electrical system
- Improves performance of the motor

Power factor improvement

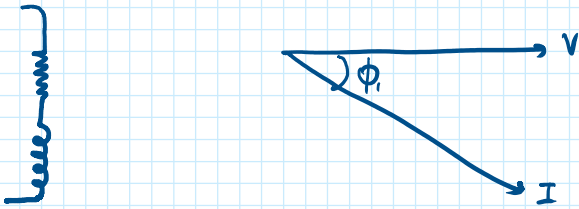

Add a capacitor to reduce lag.

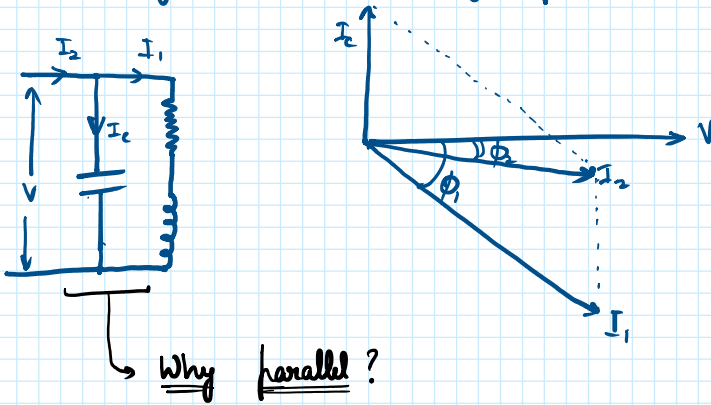Ant. of current drawn by capacitor \Rightarrow Amount of reactive power reduced



Why parallel?

Q. The load taken from AC supply consist of a heating load of 15 kW, a motor load of 40 kVA at 0.6 lag and a load of 20 kW at 0.8 lag. Calculate the load from supply in kW and kVA and its power factor. What would be the kVAR rating of a capacitor to bring the power factor to unity and how would it be connected?

Soln.

|

Soln.




Q. The power consumed in the inductive load is 2.5 W at 0.71 lagging power factor. The input voltage is 230 V, 50 Hz. Find the value of the capacitor C which must be placed in parallel, such that the resultant power factor of the input current is 0.866 lagging.

$$P_i = 2.5 \text{ W}$$

$$\cos \phi_i = 0.71$$

$$\phi_i = 44.765^\circ$$

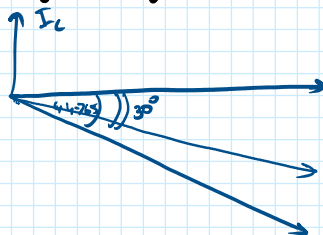

$$Q_c = \frac{V^2}{X_c}$$

$$VI = 3.52 \text{ kVA}$$

Q. A network consists of 2 branches, the 1st branch is a coil having resistance of 6 Ω and an inductance of 25.46 mH. The 2nd branch has resistance of 8 Ω connected in series with a capacitor of 530.52 μF . The supply voltage is 200 V 50 Hz. Determine:

- (i) Current in each branch
- (ii) Source current
- (iii) Active and reactive power in branch 1
- (iv) Active and reactive power in branch 2
- (v) Overall power factor of the circuit