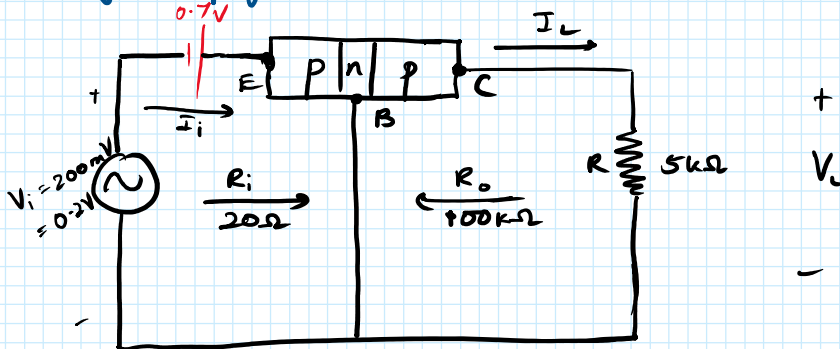


## 9. Transistor Amplifying Action, Relation b/w $\alpha$ and $\beta$

10 October 2023 15:25

### TRANSISTOR AMPLIFYING ACTION - COMMON BASE

Voltage amplification  $\rightarrow$  denoted as  $A_v$



$$I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

If we assume  $\alpha_{ac} = 1$  ( $I_c = I_e$ ),

$$I_L = I_i = 10 \text{ mA}$$

$$V_L = I_L R$$

$$= (10 \text{ mA}) (5 \text{ k}\Omega)$$

$$= \underline{\underline{50 \text{ V}}}$$

Voltage amplification  $A_v$

$$A_v = \frac{V_L}{V_i} = \frac{50 \text{ V}}{200 \times 10^{-3}} = 0.25 \times 10^3 = 250$$

range: (50-300)

Q. For the previous problem, if the input voltage is changed to 500 mV and the collector load is 1 k $\Omega$ , assuming all other parameters are the same, find the output voltage and the voltage amplification.

Soln.

$$I_i = \frac{500 \text{ mV}}{20 \Omega} = 25 \text{ mA}$$

Assuming  $\alpha = 1$

$$I_L = I_i = 25 \text{ mA}$$

$$V_L = I_L R$$

$$= (25 \text{ mA}) (1 \text{ k}\Omega)$$

$$= \underline{\underline{25 \text{ V}}}$$

Voltage amplification  $A_v$

$$A_v = \frac{V_o}{V_i} = \frac{28 \times 10^{-1}}{\frac{500 \text{ mV}}{100 \times 20}} = 0.05 \times 10^3 = \underline{\underline{500}}$$

### RELATION BETWEEN $\alpha$ AND $\beta$

w.k.t

$$\beta = \frac{I_c}{I_b}, \quad \alpha = \frac{I_c}{I_e}$$

$$\Rightarrow I_b = \frac{I_c}{\beta}, \quad I_e = \frac{I_c}{\alpha}$$

Total current

$$I_e = I_c + I_b$$

Substituting,

$$\frac{I_c}{\alpha} = I_c + \frac{I_c}{\beta}$$

Dividing by  $I_c$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta} \quad \Rightarrow \quad \frac{1}{\beta} = \frac{1}{\alpha} - 1$$

$$\boxed{\alpha = \frac{\beta}{\beta + 1}}$$

$$\boxed{\beta = \frac{\alpha}{\alpha - 1}}$$