

1. Basic circuit elements: Resistor, Inductor, Capacitor

04 September 2023 11:51

Resistor: A material that opposes the flow of current

SI unit: ohms (Ω)

Symbol: $\text{---}\frac{\text{---}}{R}\text{---}$

Inductor: That which stores the charges in the form of magnetic field

SI unit: Henry (H)

Symbol: $\text{---}\text{---}\underset{L}{\text{---}}\text{---}$

Capacitor: That which stores charges in the form of electric field

SI unit: Farad (F)

Symbol: $\text{---}\text{---}\underset{C}{\text{---}}\text{---}$

RESISTOR COLOUR CODING

6-Band $2\ 7\ 4 \cdot 10^3 \pm 2 = 274\ \Omega \pm 2\%, 250\ \text{ppm/K}$

Color	1st Digit	2nd Digit	3rd Digit	Multiplier	Tolerance	Temperature Coefficient
Black	0	0	0	1 Ω		250 ppm/K
Brown	1	1	1	10 Ω	$\pm 1\%$	100 ppm/K
Red	2	2	2	100 Ω	$\pm 2\%$	50 ppm/K
Orange	3	3	3	1k Ω		15 ppm/K
Yellow	4	4	4	10k Ω		25 ppm/K
Green	5	5	5	100k Ω	$\pm 0.5\%$	20 ppm/K
Blue	6	6	6	1M Ω	$\pm 0.25\%$	10 ppm/K
Violet	7	7	7		$\pm 0.1\%$	5 ppm/K
Grey	8	8	8			1 ppm/K
White	9	9	9			
Gold				0.1 Ω	$\pm 5\%$	
Silver				0.01 Ω	$\pm 10\%$	

4-Band $12 \times 10^3 \pm 5\% = 1,200\ \text{k}\Omega \pm 5\%$

5-Band $100 \times 10^3 \pm 1\% = 10,000\ \Omega \pm 1\%$

BASIC CIRCUIT ELEMENTS

They are of two types:

- Passive Elements:** An electronic component which can only receive energy.
- Either dissipates, absorbs or stores energy in an electric field [or] a magnetic field.
 - Do not need any form of electrical power to operate
 - Eg: Resistor, inductor, capacitor

Active Elements: Components that supply energy to the circuit

• EXAMPLES

- Voltage Source: used to create potential difference b/w two points in the circuit (eg: battery)
- Current Source: supplies current to the circuit (eg: DC current source, AC current source)
- Voltage/current sources are of two types: dependent and independent

transformer



battery

OHM'S LAW

$$V \propto I$$

$$V = IR$$

resistance: proportionality constant

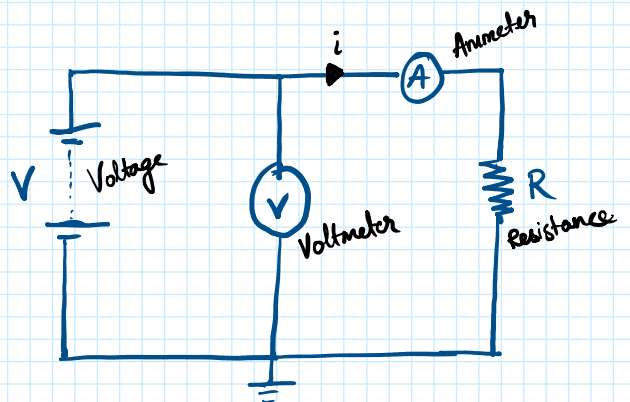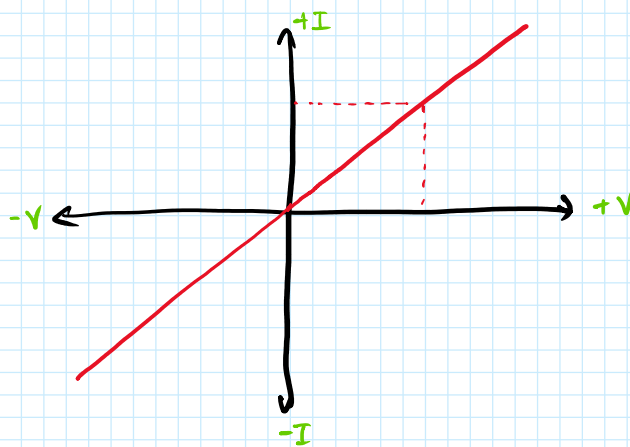


VOLTAGE - CURRENT RELATION IN CAPACITOR

Voltage is proportional to integral of current


$$V \propto \int I \, dt$$

$$V = \frac{1}{C} \int_{t_0}^t I \cdot dt$$
$$I = C \frac{dv}{dt}$$

} Doubt

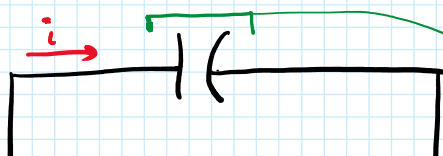

polarized capacitor: has +ve and -ve

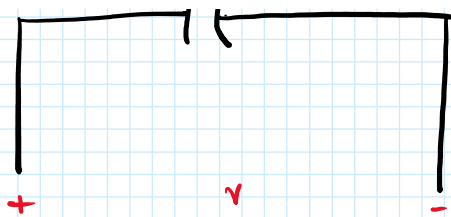

polarized capacitor: has +ve and -ve

VOLTAGE - CURRENT RELATION IN INDUCTOR

Voltage is proportional to the differential of the current in inductor


$$V \propto \frac{dI}{dt}$$

$V = L \frac{dI}{dt}$
$I_L = \frac{1}{L} \int_{t_0}^t V_L dt$

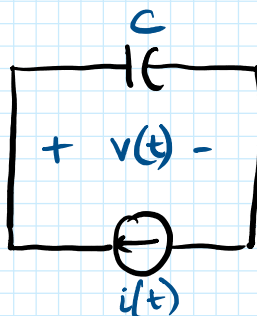PROBLEMS

- ① The input to the circuit shown in figure ① is the current $i(t) = 3.75e^{-1.2t} A$ for $t > 0$.

The output is the capacitor voltage $v(t) = 4 - 12.5e^{-1.2t} V$ for $t > 0$.
Find capacitance C .



Soln. $v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt$

$$4 - 12.5e^{-1.2t} = \frac{1}{C} \int_0^t 3.75e^{-1.2t} dt$$

$$4 - 12.5e^{-1.2t} = \frac{3.75}{C} \left[\frac{e^{-1.2t}}{-1.2} \right]_0^t$$

$$= \frac{3.75}{-1.2C} [e^{-1.2t} - 1]$$

$$= \frac{-3.125}{C} [e^{-1.2t} - 1]$$

$$4 - 12.5e^{-1.2t} = -3.125e^{-1.2t} + 3.125$$


$$4 - 12.5e^{-1.2t} = \frac{-3.125e^{-1.2t}}{C} + \frac{3.125}{C}$$

equating coefficients

$$12.5 = \frac{3.125}{C}$$

$$\Rightarrow C = \frac{3.125}{12.5} = \underline{\underline{0.25 \text{ F}}}$$

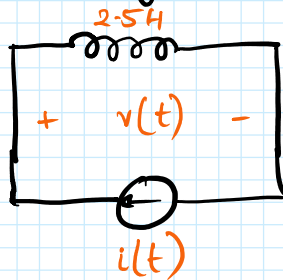- ② Input to given circuit is $i(t) = 3 - 4.5e^{-6t} \text{ A}$ for $t > 0$.
Determine the inductor voltage $v(t)$ for $t > 0$



Soln: $v(t) = L \frac{di}{dt}$

$$v(t) = (2.5) \frac{d}{dt} (3 - 4.5e^{-6t})$$

$$= (2.5)(-4.5)(-6)e^{-6t}$$

$$v(t) = \underline{\underline{67.5e^{-6t}}}$$

say for $t=1$,

$$v(t) = \underline{\underline{0.167 \text{ V}}}$$