

2. Boolean Laws, Realisation of Boolean Gates using Universal Gates

07 November 2023 14:46

BOOLEAN LAWS

Inversion law

$$\begin{aligned} \text{If } A = 1 &\longrightarrow A' = 0 \\ A = 0 &\longrightarrow A' = 1 \end{aligned}$$

Double Inversion law

$$(A')' = A$$

AND law

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot A' = 0$$

OR law

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + A' = 1$$

Principle of duality / Duality theorem

- Each AND sign is changed to an OR sign, 0s are changed to 1s and vice versa for both.

Dual of AND gate \Rightarrow OR gate

$$A \cdot B \Rightarrow A + B$$

Dual of NAND gate \Rightarrow NOR gate

$$\overline{A \cdot B} \Rightarrow \overline{A + B}$$

Dual of XOR gate \Rightarrow XNOR gate

Commutative law

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

Associative law

$$(A + B) + C = A + (B + C)$$

From principle of duality:

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

Distributive law

$$A + B \cdot C = (A+B) \cdot (A+C)$$

$$A + \bar{A} \cdot B = (A + \bar{A}) \cdot (A + B) = A + B$$

redundant

$$\bar{A} + A \cdot \bar{B} = \bar{A} + \bar{B}$$

redundant

From principle of duality,

$$A \cdot (B+C) = A \cdot B + A \cdot C$$

De Morgan's Theorem

"Break the line, change the sign"

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

Absorption Theorem

(i) $A + AB = A$

$$\therefore A + AB = A(1+B)$$

$\xrightarrow{=1}$

$$\Rightarrow A + AB = A$$

(ii) $A(A+B) = A$

$$A \cdot A + A \cdot B$$

$\xrightarrow{=A}$

$$\Rightarrow A + AB = A(1+B) = A$$

$\xrightarrow{=1}$

Redundancy Laws

(i) $A + \bar{A}B = A + B$

(ii) $A \cdot (\bar{A} + B) = AB$

$$A + \bar{A} \cdot B = (A + \bar{A}) \cdot (A + B) = A + B$$

redundant since $(A + \bar{A})$ is 1

Consensus Theorem

$$Y = AB + \bar{B}C + \bar{A}C = AB + \bar{A}C$$

redundant

$$AB + \bar{A}C + \bar{B}C(A + \bar{A})$$

If you have an expression with no single variable:

- Check terms for any variable X and

$$\begin{aligned}
 & AB + \bar{A}\bar{C} + BC(A + \bar{A}) \\
 &= AB + \bar{A}\bar{C} + ABC + \bar{A}\bar{B}C \\
 &= AB + ABC + \bar{A}\bar{C} + \bar{A}\bar{B}C \\
 &= AB(1+C) + \bar{A}\bar{C}(1+B) \\
 &= AB + \bar{A}\bar{C}
 \end{aligned}$$

redundant since both equal one

Example

$$\begin{aligned}
 \textcircled{1} \quad Y &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{B}C + \bar{A}\bar{B} + AC \\
 &= \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{B} + AC \\
 &= \bar{A}\bar{B} + \bar{B}\bar{C} + AC
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{2} \quad Y &= AB + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC \\
 &= AB + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC \\
 &= AB(1+C) + \bar{A}\bar{B}(1+C) + \bar{A}\bar{C}(1+B) \\
 &= AB + \bar{A}\bar{B} + \bar{A}\bar{C}
 \end{aligned}$$

UNIVERSAL GATES


NAND

NOR

- Any digital logic circuit can be implemented using these


REALISATION OF LOGIC GATES USING NAND

① NOT GATE

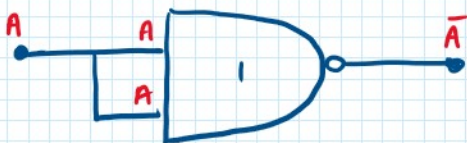

$$Y = \overline{A \cdot A} = \bar{A} + \bar{A} = \bar{A}$$

② AND GATE

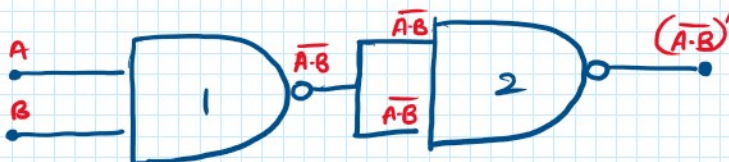

$$Y = (\bar{A}\bar{B})' = AB$$


③ OR GATE

variable.

- Check terms for any variable X and its complement \bar{X} .
- If such terms exist, then check their coefficients.
Eg: $XA, \bar{X}B$
Coefficients: A, B
- Check for terms consisting of only the coefficient variables (eg: AB).
Such terms are taken as redundant




REMEMBER: A P P L E

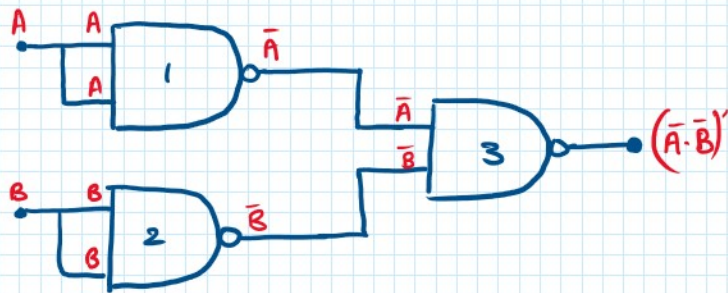

$$Y = (\bar{A} \cdot \bar{B})' = (\overline{A+B})'$$


$$Y = A+B$$

④ NOR GATE

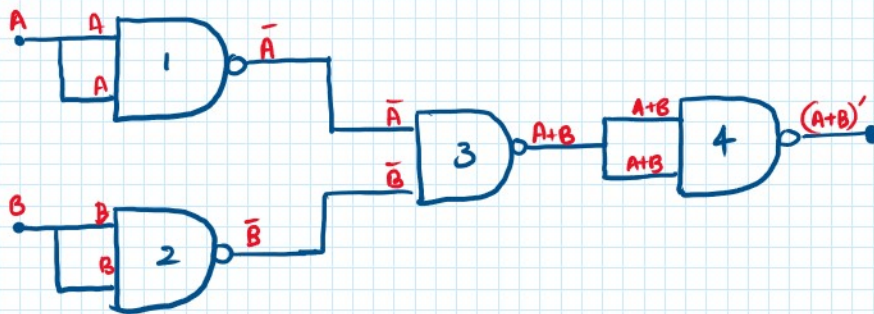

$$Y = \overline{A+B}$$

⑤ XOR GATE

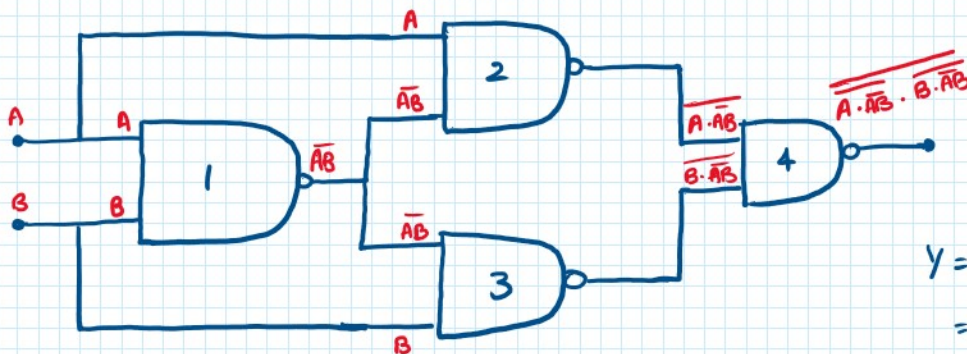

$$Y = \overline{A \cdot \bar{A} B \cdot B \cdot \bar{A} B}$$

$$= \overline{A \cdot \bar{A} B} + \overline{B \cdot \bar{A} B}$$


$$= A \cdot \bar{A} B + B \cdot \bar{A} B$$

$$= A \cdot \bar{A} B + B \cdot \bar{A} B$$

$$= A \cdot (\bar{A} + B) + B \cdot (\bar{A} + B)$$

$$= A \bar{B} + \bar{A} B$$

⑥ XNOR GATE

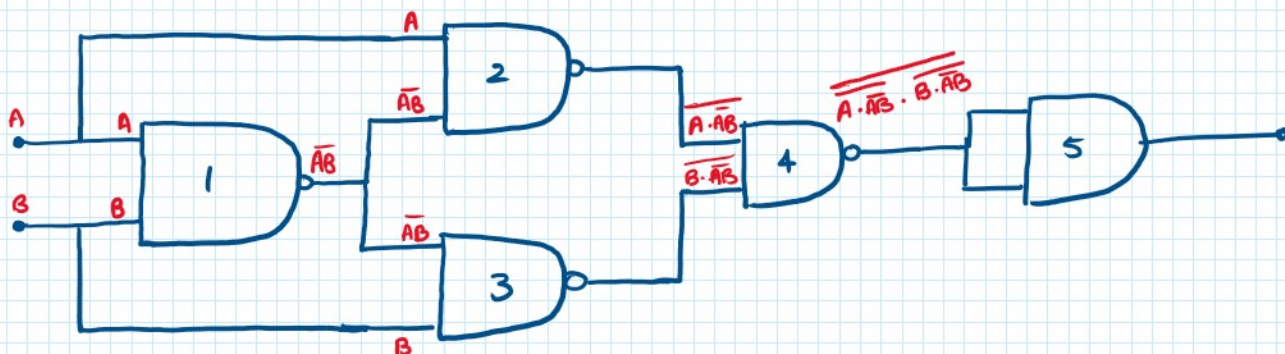

REALISATION OF LOGIC GATES USING NOR

NOT - 1

OR - 2


AND - 3

NAND - 4

XOR - 5

XNOR - 4


① NOT GATE

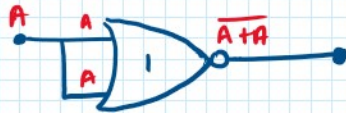

$$Y = \overline{A+A} = \overline{A} \cdot \overline{A}$$


$$Y = \overline{A}$$

② OR GATE

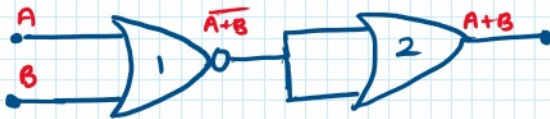

$$Y = A+B$$

③ AND GATE

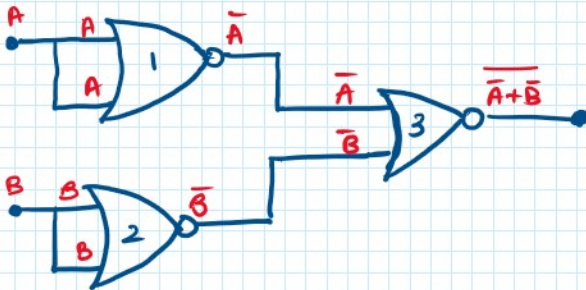


$$Y = \overline{\overline{A} + \overline{B}}$$

$$= \overline{\overline{A \cdot B}}$$

$$Y = A \cdot B$$

④ NAND GATE

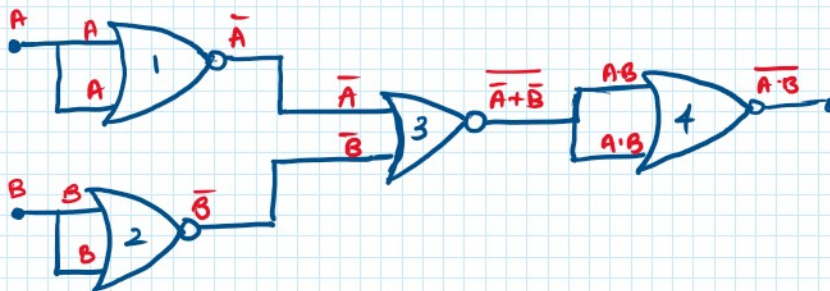


$$Y = \overline{\overline{\overline{A+B}}}$$


$$= \overline{\overline{A \cdot B}}$$

$$= \overline{A \cdot B}$$

⑤ XOR GATE

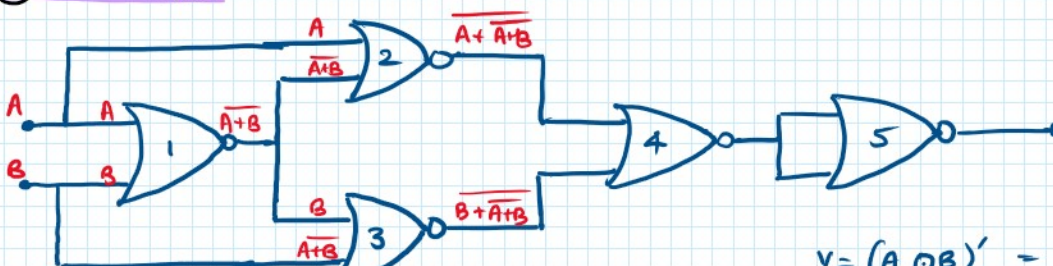


$$Y = (A+B+A \cdot B)' = A \oplus B$$

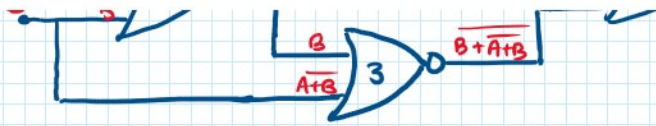

$$Y = (A \cup B)' = A \oplus B$$

⑥ XNOR GATE

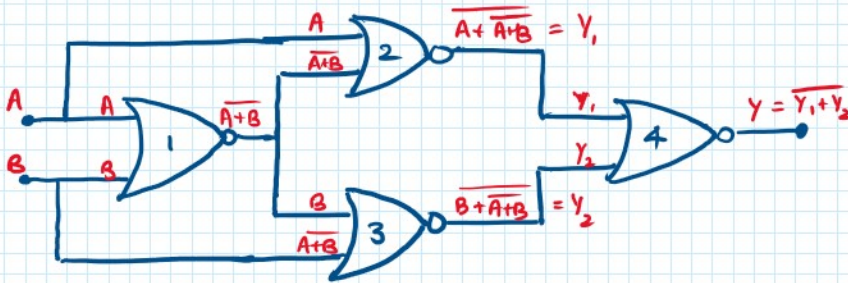

$$\begin{aligned} Y_1 &= \overline{A + A + B} \\ &= \overline{A} \cdot \overline{A + B} \\ &= \overline{A} (A + B) \\ &= \overline{A} B \end{aligned}$$

$$\begin{aligned} Y_2 &= \overline{B + A + B} \\ &= \overline{B} \cdot \overline{A + B} \\ &= \overline{B} (A + B) \\ &= A \overline{B} \end{aligned}$$

$$Y = \overline{A} B + A \overline{B}$$


PROBLEMS

① Realise $F = XY + Z$ using only NAND gates


Solution:

Method ①


Step ①: Draw basic gates expression

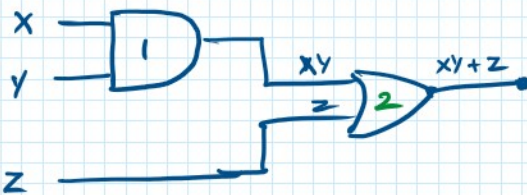

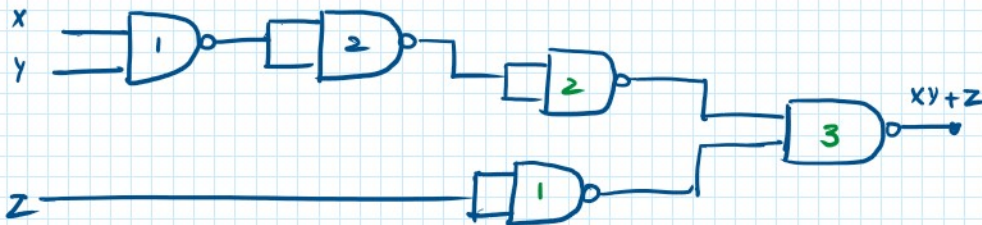
Step ②: Replace each gate by its NAND equivalent



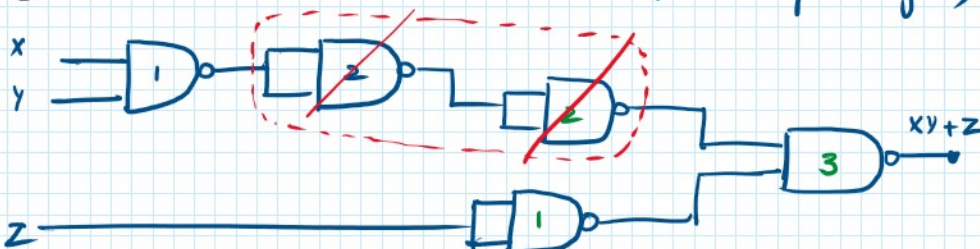Step ③: Remove double successive inversions (doubled up NOT gates)




Solution:



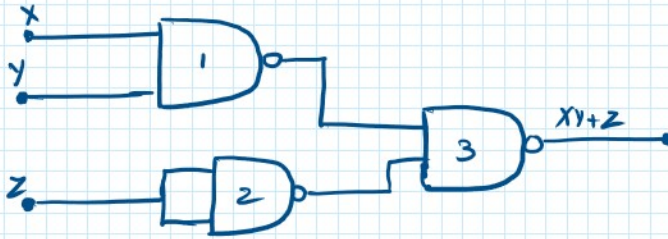


Method (2)

Step ①: Draw basic gate expression

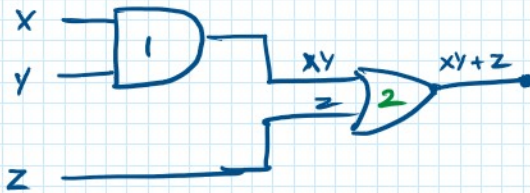

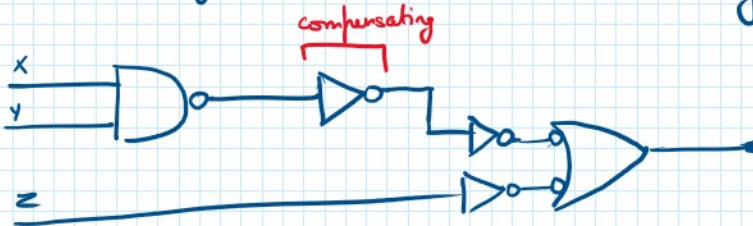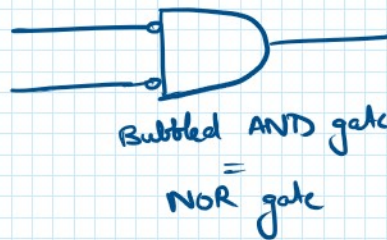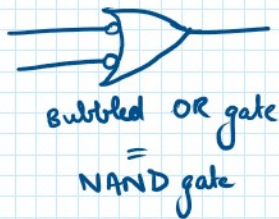Step ②: Replace each gate symbol with NAND gate symbol



Step ③: Remove double successive inversions and ensure every diode is in terms of NAND