


5. Bistable State

21 November 2023 14:42

S	R	Q	\bar{Q}	Status
0	0	0	1	Assume initial reset (No change)
0	1	0	1	Reset
1	0	1	0	Set
0	0	1	0	No change (Memory)
1	0	1	0	Set
0	1	0	1	Reset
1	1	1*	1*	Invalid / Forbidden

\bar{S}	\bar{R}	Q	\bar{Q}	Status
1	1	0	1	Assume initial reset (No change)
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	1	No change (memory)
1	0	0	1	Reset
0	1	1	0	Set
0	0	1*	1*	Invalid / Forbidden / Undefined / Uncertain

GATED / CLOCKED S-R FLIP FLOP


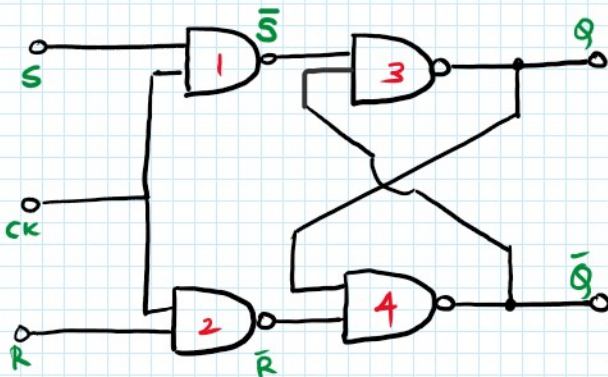


CLK	S	R	Q	\bar{Q}	Status
0	X	X	Q	\bar{Q}	No change (memory)
1	0	0	Q	\bar{Q}	No change (memory)
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	1*	1*	Invalid / Forbidden

Problems

CLK	S	R	Q	\bar{Q}	Status
0	1	0	0	1	No change (memory)
0	0	1	0	1	No change (memory)
1	0	1	0	1	Reset
0	0	0	0	1	No change (memory)
1	0	1	0	1	Reset
1	1	0	1	0	Set
0	1	0	1	0	No change (memory)
1	1	0	1	0	Set

DATA (D) Flip-Flop

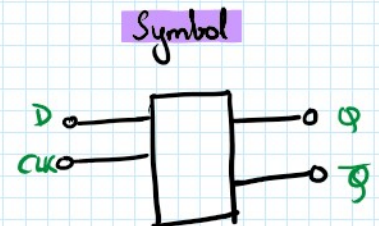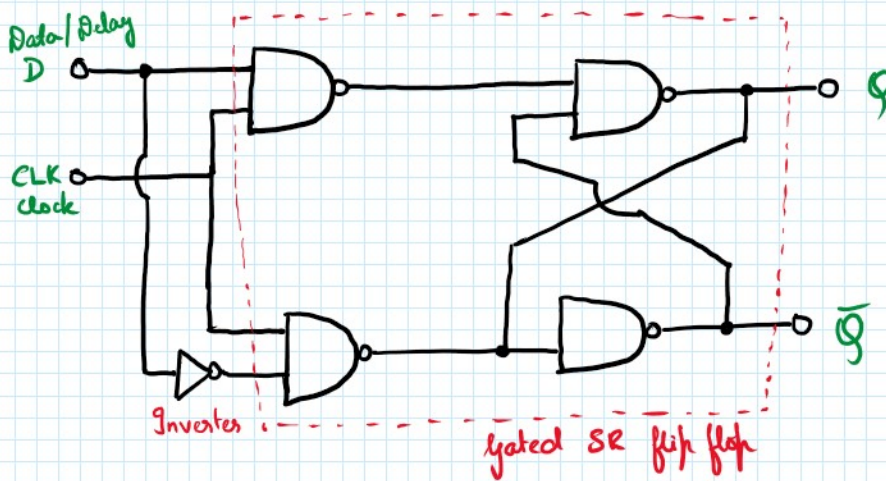


CLK	D	Q	\bar{Q}	Status
0	x	Q	\bar{Q}	Memory
1	0	0	1	Reset
1	1	1	0	Set


JK Flip-Flop (POSITIVE EDGE TRIGGERED)

inventor: Jack Kilby




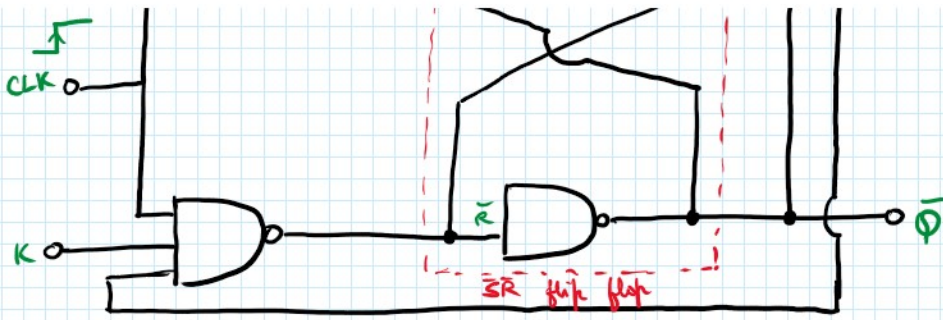


① Level Triggered


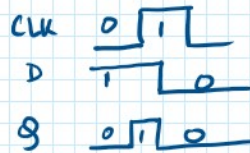


② Edge Triggered

Positive ET (PT)

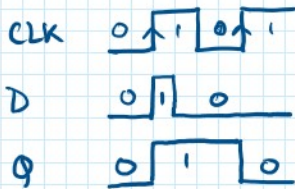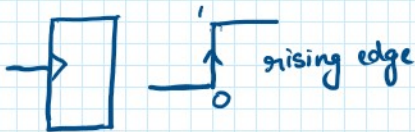

Negative ET (NT)

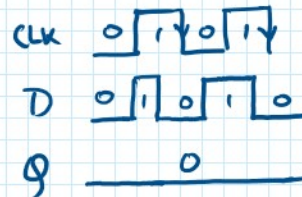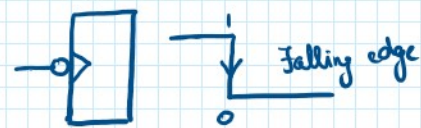

CLK	J	K	Q	Q̄	Status
1 → 0: \downarrow on \downarrow	X	X	Q	Q̄	Memory
0 → 1: \uparrow on \uparrow	0	0	Q	Q̄	Memory
0 → 1: \uparrow on \uparrow	0	1	0	1	Reset
0 → 1: \uparrow on \uparrow	1	0	1	0	Set
0 → 1: \uparrow on \uparrow	1	1	Q̄	Q	Toggle

We assume values of Q, Q̄

Q = 0 → 0

Q̄ = 1 → 1

Q = 1 → 0

Q̄ = 0 → 1

We assume values of Q, Q̄



Q = 0 → 1

Q̄ = 1 → 0

Q = 1 → 1

Q̄ = 0 → 0

T (TOGGLE) FLIP FLOP

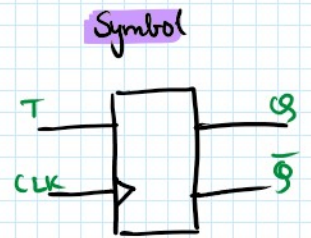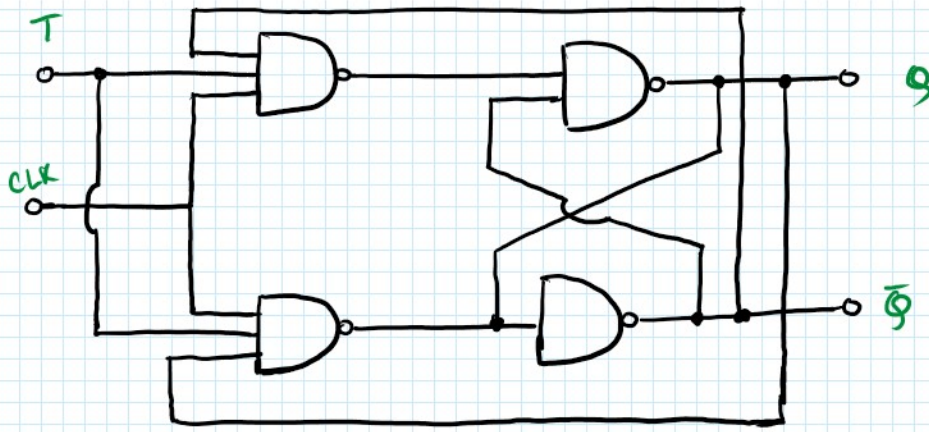

CLK	T	Q	\bar{Q}	Status
0:↓	X	Q	\bar{Q}	No change
1:↑	0	Q	\bar{Q}	No change
1:↑	1	\bar{Q}	Q	Toggles