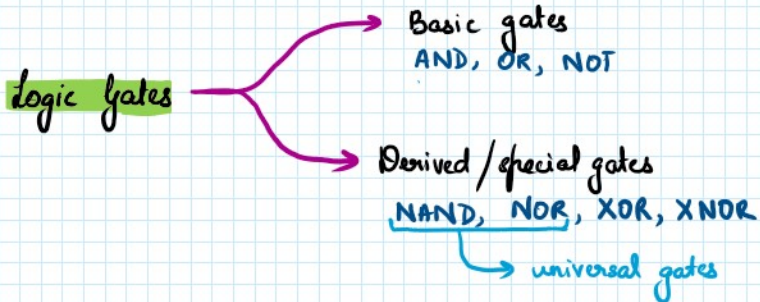


1. Boolean Algebra & Logic Gates

07 November 2023 09:39

BOOLEAN ALGEBRA, LOGIC GATES - INTRO


- Mathematics used to analyse and simplify logic/digital circuits \rightarrow boolean algebra
- Digital circuits \rightarrow constructed using logic gates
- Logic gates: one or more inputs, only one output
- Number of possible input states = $2^n \rightarrow$ no. of inputs



AND GATE

All inputs are 1 \rightarrow output is 1

$$Y = A \cdot B$$

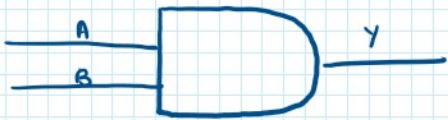

Truth Table


INPUTS		OUTPUT
A	B	Y
0	1	0
0	0	0
1	1	1
1	0	0

OR GATE

Any input is 1 \rightarrow Output is 1

$$Y = A + B$$



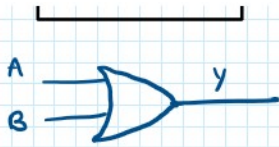

Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT GATE

Any one input \rightarrow opposite output

$$Y = \bar{A}$$




Truth Table

INPUT	OUTPUT
A	Y
0	1
1	0

NAND GATE

NOT (AND) = NAND.

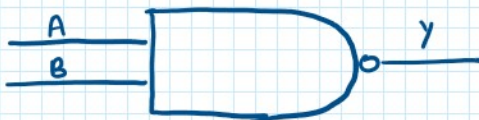Active low: If any input is 0 \rightarrow Output is 1



Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE

NOT (OR) = NOR

Active high: If any input is 1 \longrightarrow output is 0



Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

NOTE: Active high, active low

low, high \longrightarrow refers to the input the gate is "active" for

active \longrightarrow if the gate gets a certain input, not necessary to look at the other to get output, i.e., gate actively looks for certain input

XOR GATE

ODD function gate: If there is an odd no. of 1s in input \longrightarrow Output is 1

Truth Table

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

combination of inputs in SOP that give output as 1

MINTERMS: $\bar{A}B + A\bar{B}$


MAXTERMS: $(\bar{A} + \bar{B})(A + B)$

combination of inputs in POS that give output as 0

$$Y = \bar{A}B + A\bar{B}$$

$$Y = A \oplus B$$

Symbol

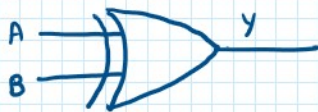


NOTE:

XOR gate performs modulo sum operation without including carry.
 $0+0=0$, $1+0=1$, $0+1=1$, $1+1=0$

3- INPUT XOR GATE

INPUTS			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0
1	0	1	0
0	1	1	0
1	1	1	1

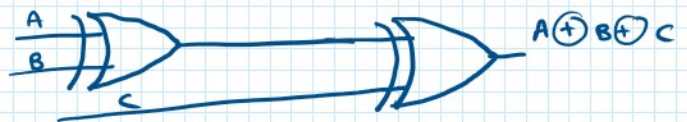

Associative law

$$(A \oplus B) \oplus C = A \oplus (B \oplus C)$$

$$\begin{aligned}
 Y &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \quad \left\{ \text{SOP form (sum of products)} \right. \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\
 &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\
 &= \bar{A}x + A\bar{x} \\
 &= A \oplus x \\
 &= \underline{\underline{A \oplus B \oplus C}}
 \end{aligned}$$

PROPERTIES OF XOR GATE

- Identity element: $A \oplus 0 = A$
- $A \oplus 1 = A'$
- $A \oplus A = 0$
- $A \oplus \bar{A} = 1$
- Commutative law: $A \oplus B = B \oplus A$

- Associative law: $A \oplus (B \oplus C) = (A \oplus B) \oplus C$

XNOR GATE

not of XOR


EVEN function gate: Even no. of 1s \rightarrow Output is 1

Truth Table

INPUTS		OUTPUT y	MINTERMS M(A,B)	MAXTERMS m(A,B)
A	B			
0	0	1	$\bar{A}\bar{B}$	-
0	1	0	-	$A+\bar{B}$
1	0	0	-	$\bar{A}+B$
1	1	1	AB	-

$$Y = A \cdot B + \bar{A} \cdot \bar{B}$$

$$Y = A \odot B$$

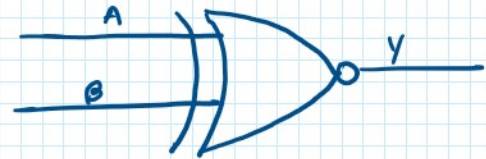

THREE INPUT XNOR GATE

INPUTS			OUTPUT Y	MINTERMS M(A,B)	MAXTERMS m(A,B)
A	B	C			
0	0	0	1	ABC	-
1	0	0	0	-	$\bar{A}+B+C$
0	1	0	0	-	$A+\bar{B}+C$
0	0	1	0	-	$A+B+\bar{C}$
1	1	0	1	$AB\bar{C}$	-
0	1	1	1	$\bar{A}BC$	-
1	0	1	1	$A\bar{B}C$	-
1	1	1	0	-	$\bar{A}+\bar{B}+\bar{C}$

APPLICATIONS OF XOR AND XNOR

- To generate parity bits and error detection
- Equality detection
- XOR gate is used in processors' ALU (Arithmetic Logic Unit) for binary addition
- XOR gate is used to generate pseudorandom numbers