

3. Types of Power, R-C Circuit, LCR Circuit

01 March 2024 09:01

Types of Power

- Pure inductor/capacitor $\rightarrow P_{avg} = 0$
Power circulates from source to load and vice versa, is not consumed. } Reactive power
- Inductor, capacitor \rightarrow reactive elements $Q = VI \sin \phi$
- Denoted by Q , units: VAR

- Apparent power
Product of RMS value of voltage & current \rightarrow apparent power
- Denoted by S , units: VA

Resistor: Power absorbed is consumed

Reactive power = 0


Inductor/Capacitor: Power consumed is zero

Active power = 0

Active Power

Power consumed by the load, denoted by P , units: Watts


Power Factor

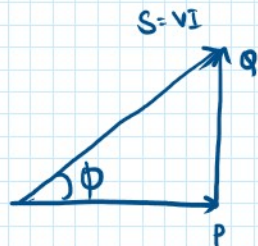


Ratio of active power to apparent power \rightarrow power factor

$$\text{Power factor} = \frac{P}{S} = \cos \phi$$

SERIES R-C CIRCUIT RESPONSE

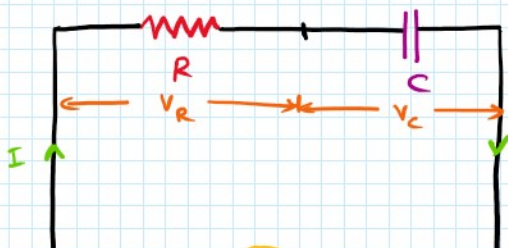

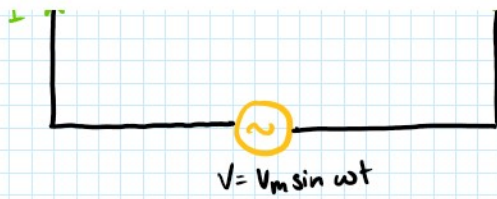


$$\bar{V} = \bar{V}_R + \bar{V}_C$$



$$V = \sqrt{(IR)^2 + (IX_C)^2}$$

$$V = I \sqrt{R^2 + X_C^2} \rightarrow Z$$

$$Z = \sqrt{R^2 + X_C^2}$$

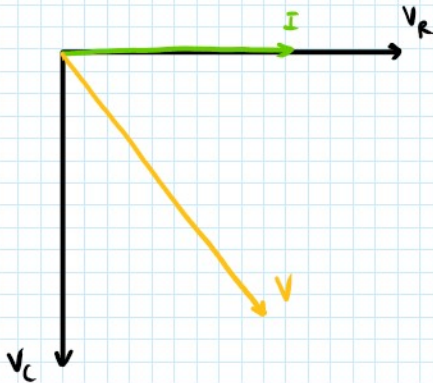

SERIES LCR CIRCUIT RESPONSE

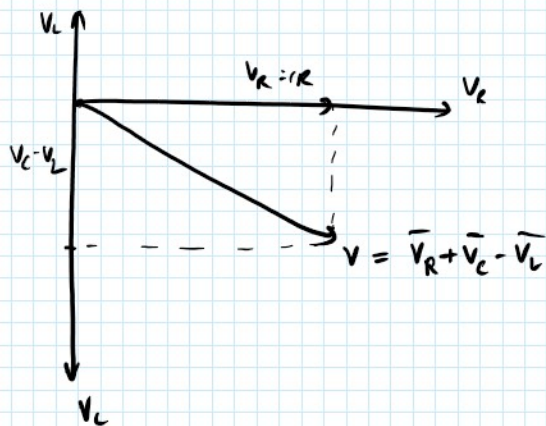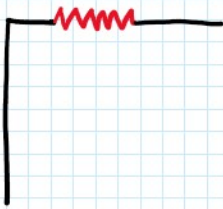

POWER EXPRESSIONS : SUMMARY

Element/Network	Phase Angle	Active Power $P = VI \cos \phi$	Reactive Power $Q = VI \sin \phi$	Apparent Power $S = VI$
R	0°	VI	0	VI
L	90°	0	VI	VI
C	-90°	0	$-VI$	VI
Series RL Circuit	$\tan^{-1}\left(\frac{X_L}{R}\right)$	$VI \cos \phi$	$VI \sin \phi$ (+ve)	VI
Series RC Circuit	$-\tan^{-1}\left(\frac{X_C}{R}\right)$	$VI \cos \phi$	$VI \sin \phi$ (-ve)	VI

NUMERICALS

① Series RL circuit is connected to a sinusoidal voltage source $v(t) = 100 \sin(\omega t)$ V. It draws a current of $10 \sin(\omega t - 60^\circ)$ A. Determine:

(i) Active, reactive, apparent power

(ii) Power factor of the circuit

Soln: $V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}}$ V

$$I = \frac{I_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} \text{ V}$$

$$\phi = \angle \bar{V} - \angle \bar{I} = 0^\circ - (-60^\circ) = 60^\circ$$

$$P = VI \cos \phi = \frac{1000}{1} = 250 \text{ W}$$

$$Q = VI \sin \phi = \frac{1000}{2} \sin 60 = 433.012 \text{ VAR}$$

$$S = VI = \frac{1000}{2} = 500 \text{ VA}$$

$$\text{Power factor} = \frac{P}{S} = \cos 60 = \frac{1}{2} \text{ lag}$$