
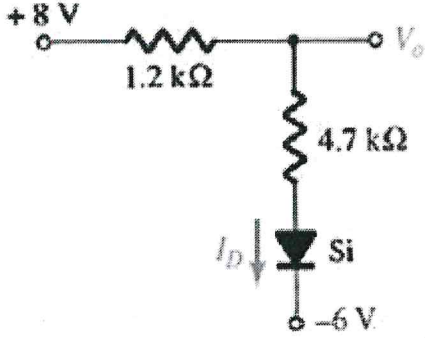
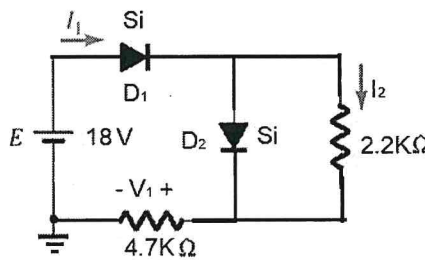


Time: 180 mins		Answer All Questions		Max Marks: 100
1.	a	Give the Difference between the following. (i) Avalanche Breakdown and Zener Breakdown (ii) Static Resistance and Dynamic Resistance (iii) Ideal diode and Practical diode		6M
	b	Solve the following using second approximation for a diode. (i) Determine V_o and I_D  (ii) Determine I_1 , I_2 and V_1 for the circuit shown in the Figure below 		8M
	c	Using Shockley's equation, Find the diode current I_d for a silicon Diode, if the applied voltage $V_D=0.71$ and Reverse Saturation Current is 4×10^{-12} A at a temp of 30° C. Consider ($\eta=1$).		6M
2.	a	With a neat circuit diagram and waveforms explain Half wave Rectifier		6M
	b	Derive the expression for I_{dc} , I_{rms} and hence find the Efficiency for Full wave Rectifier		8M
	c	Determine the range of values of V_i that will maintain the Zener diode in the “on” state.		6M

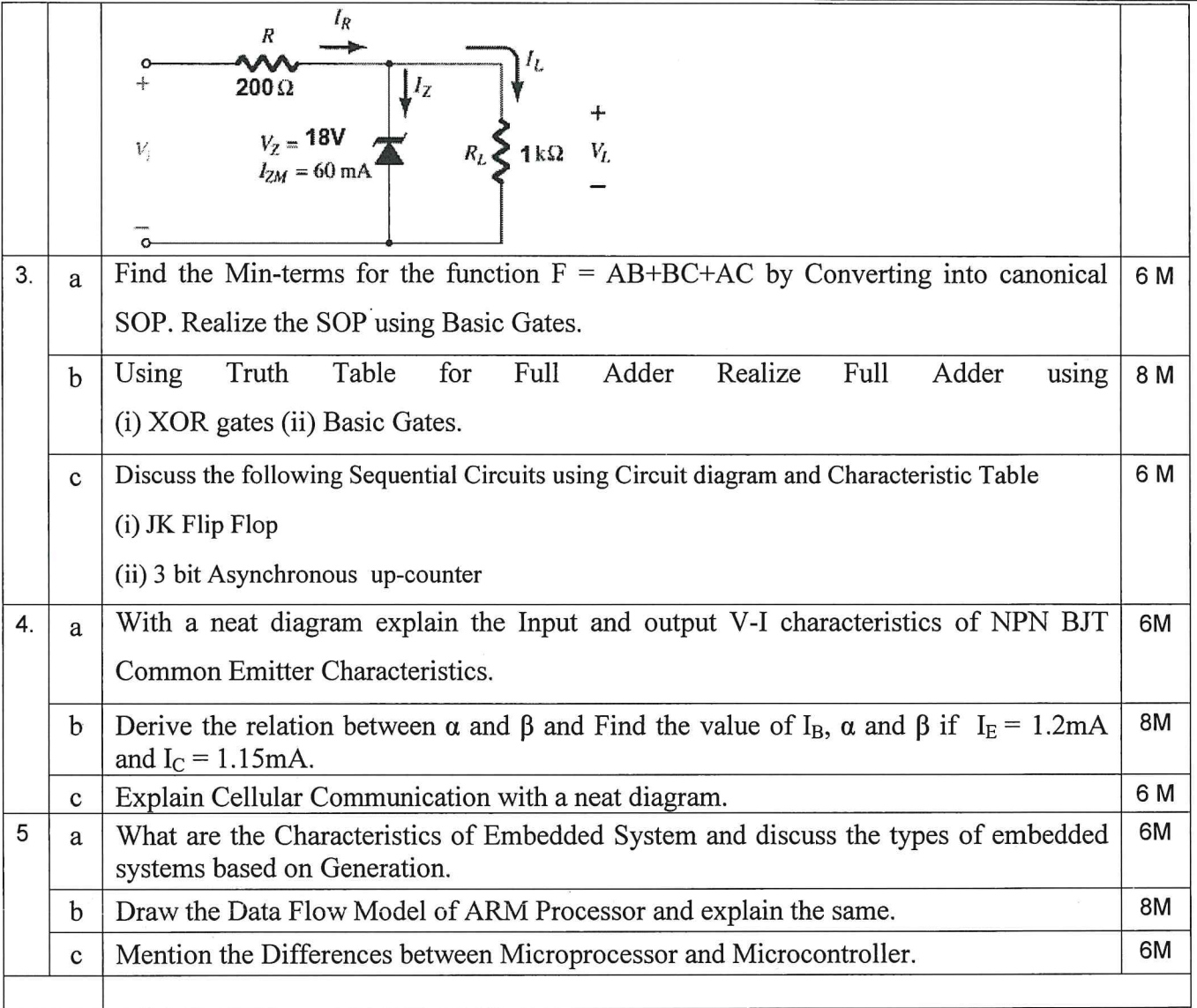

c	Mention the Differences between Microprocessor and Microcontroller.	6M
---	---	----