



PES
UNIVERSITY

ELECTRONIC PRINCIPLES AND DEVICES

Department of Electronics and Communication.


ELECTRONIC PRINCIPLES AND DEVICES

Semiconductor Diode applications

Department of Electronics and Communication.


ELECTRONIC PRINCIPLES AND DEVICES

Regulated Power Supply

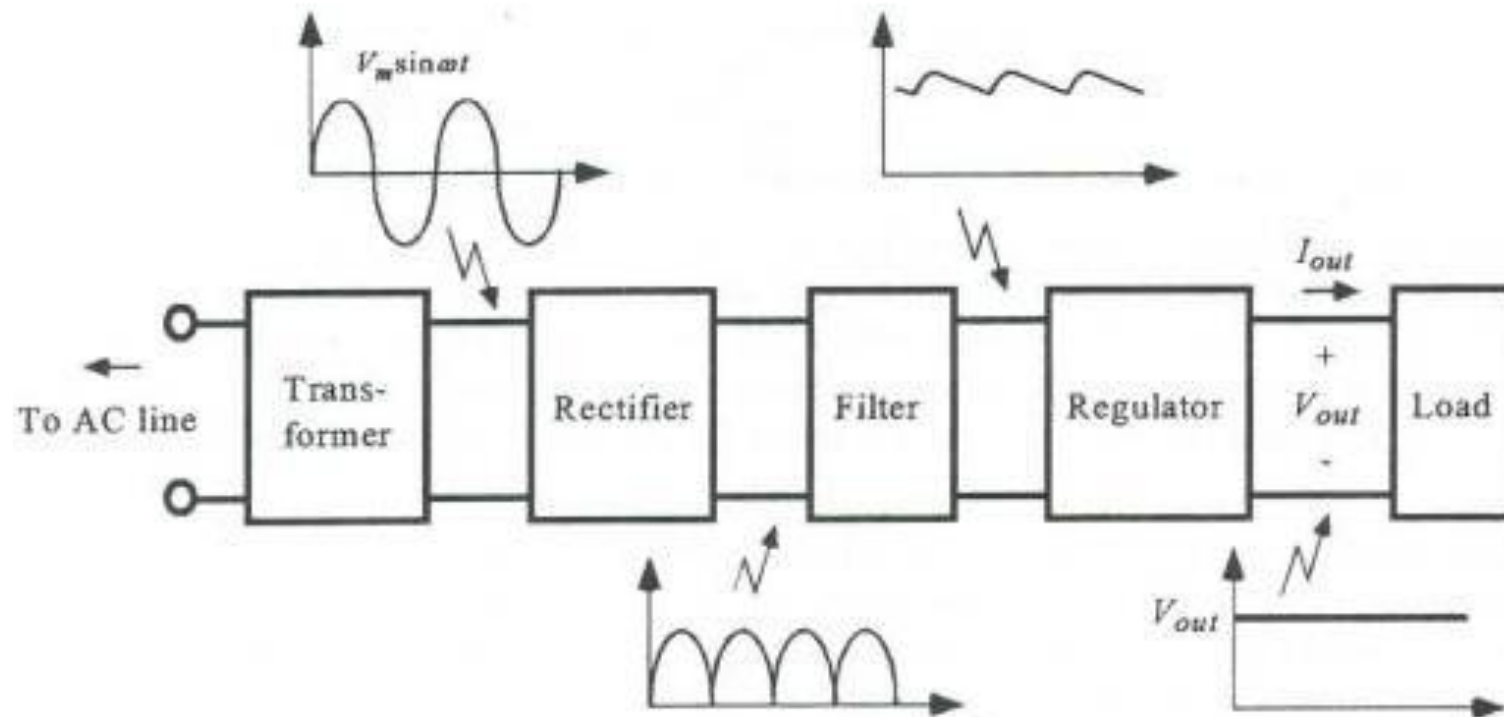

Regulated power supply converts an alternating current signal to a constant signal.


- **Transformer** : The output sinusoidal voltage is either step-up or step-down from the input sinusoidal voltage value
- **Rectifier** : Converts an alternating current into a direct one by allowing the current to flow through it in one direction only.
- **Filter** : Removes the AC ripples from the DC signal obtained from the rectifier.
- **Regulator** : Converts DC voltage into a lower constant voltage

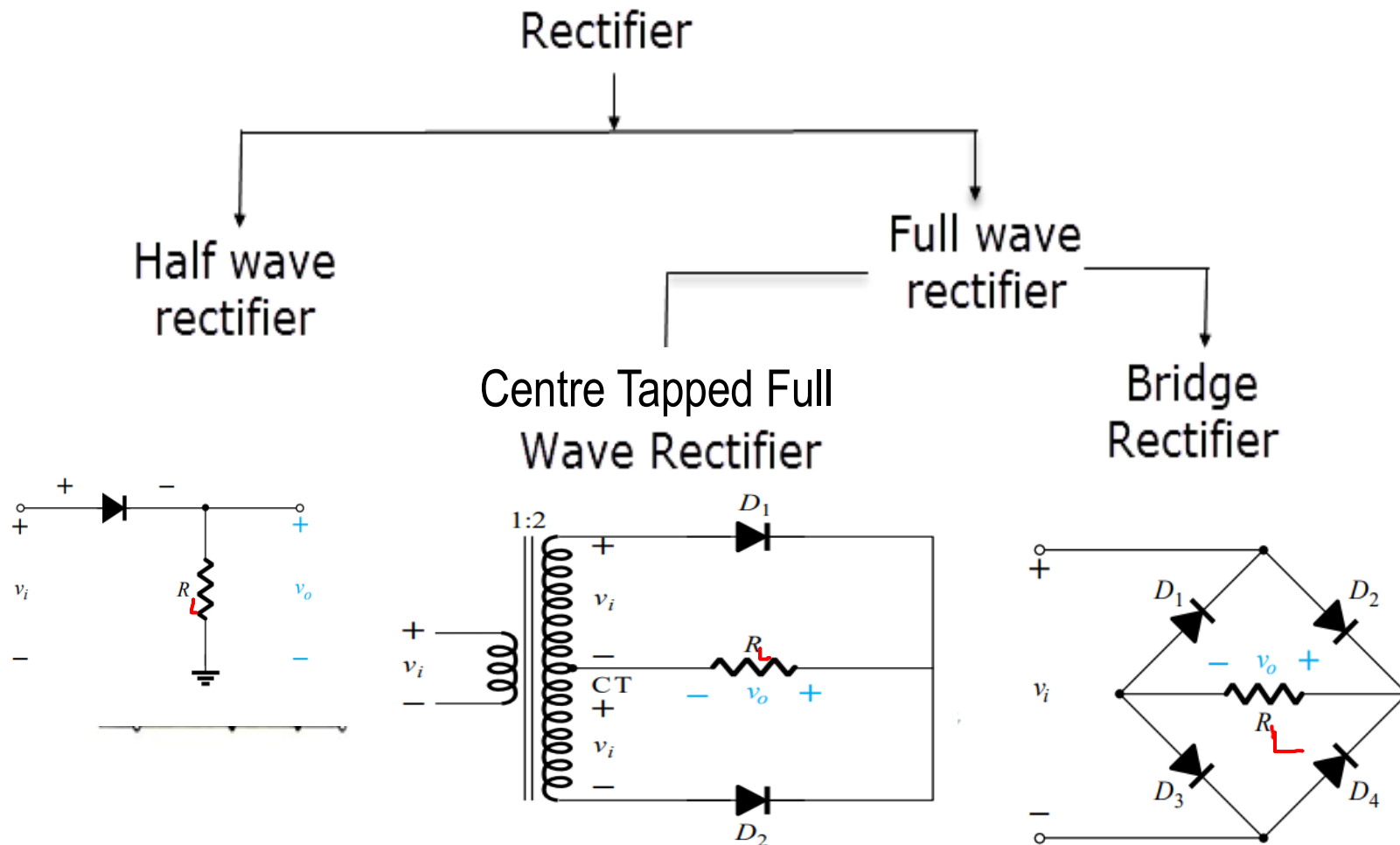


ELECTRONIC PRINCIPLES AND DEVICES

Half Wave Rectifier (HWR) - Ideal Diode


Input Waveform

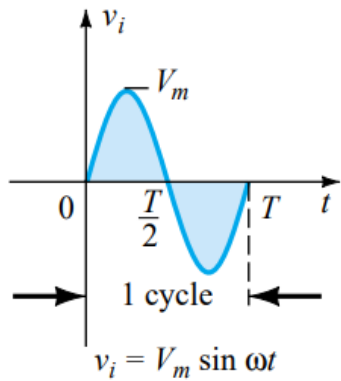


HWR Circuit

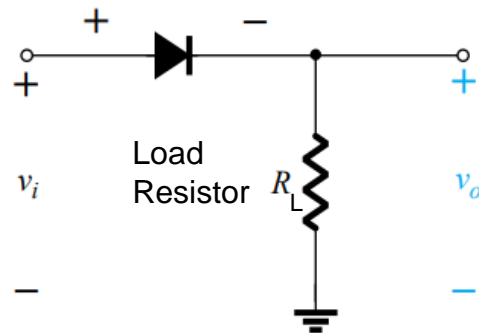

Positive Half Cycle:

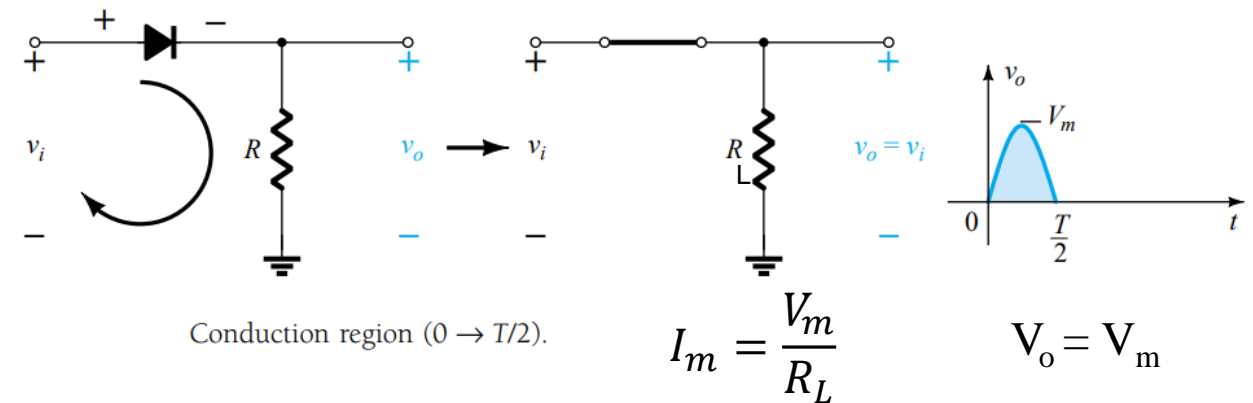


Negative Half Cycle:

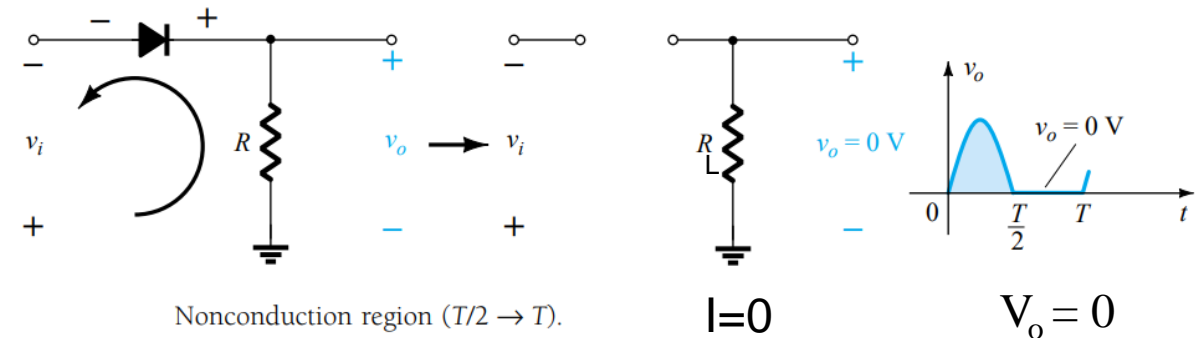

ELECTRONIC PRINCIPLES AND DEVICES


Half Wave Rectifier (HWR) - Ideal Diode

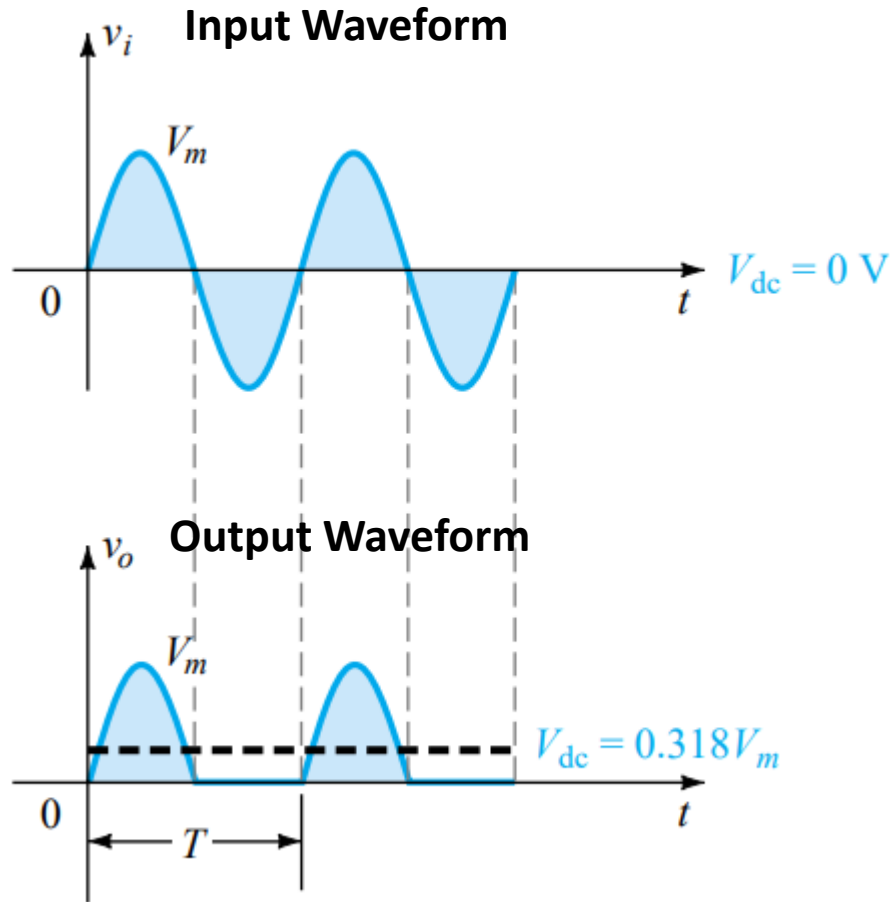



ELECTRONIC PRINCIPLES AND DEVICES

Half Wave Rectifier (HWR) - Non Ideal Diode

Positive Half Cycle:

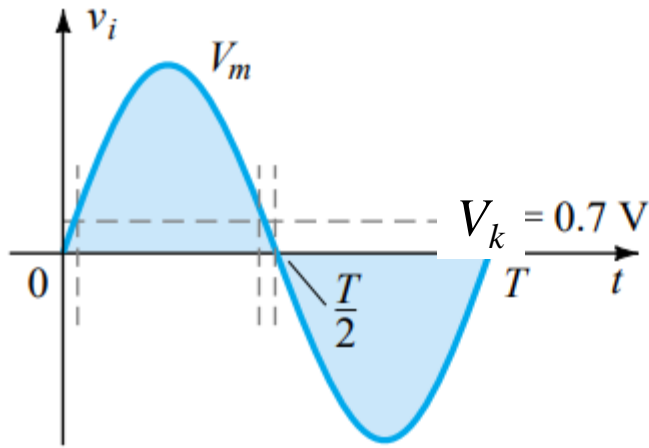

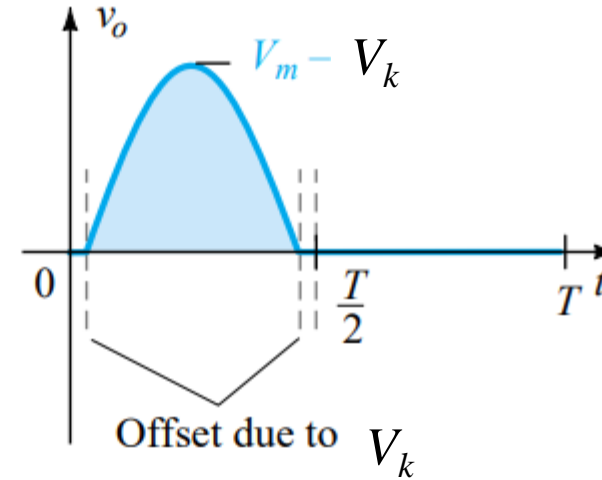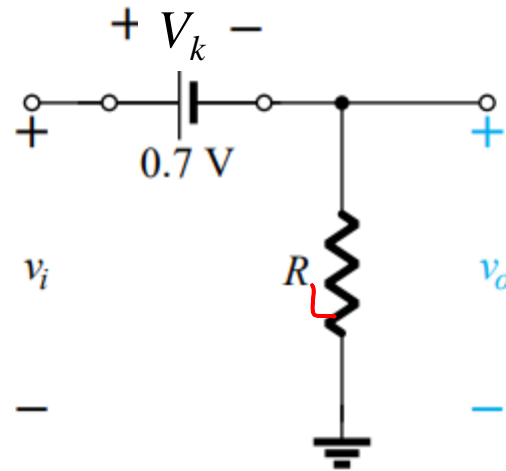
Effect of V_k on half-wave rectified signal.



$$V_{\text{omax}} = V_m - V_k$$

$$I_{\text{omax}} = \frac{V_m - V_k}{R_l}$$

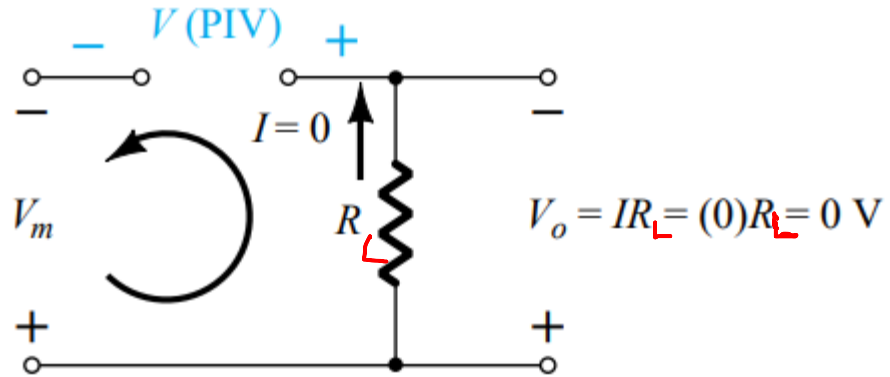Half Wave Rectifier (HWR) PIV - Ideal Diode & Non Ideal Diode




$$\text{PIV rating} \geq V_m$$

half-wave rectifier



Peak Inverse Voltage (PIV) or Peak Reverse voltage (PRV)- (For both Ideal & Non-Ideal) is the maximum reverse biased voltage (V_m) the diode can withstand without entering the breakdown region.

$$\begin{aligned} V_{dc} &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \, d\omega t \\ &= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_0^{\pi} = \frac{V_m}{\pi} \end{aligned}$$
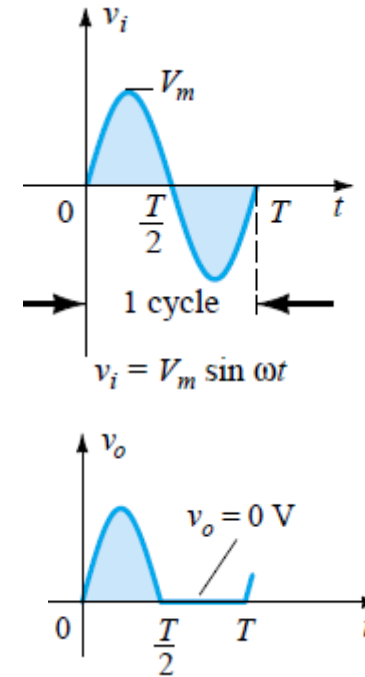
$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{V_m}{\pi R_L} = \frac{I_m}{\pi}$$



$$\begin{aligned} V_{rms} &= \left[\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 d\omega t \right]^{1/2} \\ &= \left[\frac{V_m^2}{2\pi} \int_0^{\pi} (\sin^2 \omega t) d\omega t \right]^{1/2} \\ &= \left[\frac{V_m^2}{2\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]^{1/2} \\ V_{rms} &= \left[\frac{V_m^2}{2\pi} \left(\frac{\omega t}{2} - \frac{\sin 2\omega t}{2} \right) \right]_0^{\pi}^{1/2} = \frac{V_m}{2} \end{aligned}$$

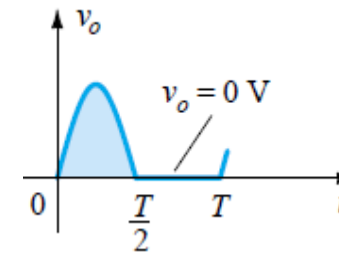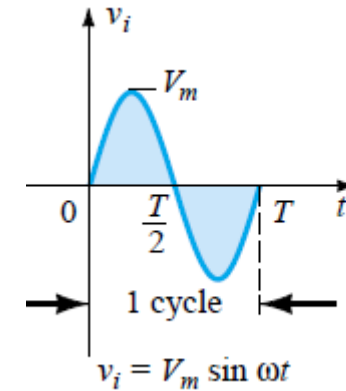

$$I_{rms} = \frac{V_{rms}}{R_L} = \frac{V_m}{2R_L} = \frac{I_m}{2}$$

$$V_{dc} = \frac{V_m - V_k}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{V_m - V_k}{\pi R_L} = \frac{I_m}{\pi} \quad \left(I_m = \frac{V_m - V_k}{R_L} \right)$$

$$V_{rms} = \frac{V_m - V_k}{2}$$

$$I_{rms} = \frac{V_{rms}}{R_L} = \frac{V_m - V_K}{2R_L} = \frac{I_m}{2} \quad \left(I_m = \frac{V_m - V_k}{R_L} \right)$$

Ripple Factor is a measure of purity of the dc output of a rectifier and can be defined as

$$r = \frac{\text{rms value of the ac component of the output}}{\text{average or dc value of the output}}$$


$$\text{Ripple Factor } (Y_{HWR}) = \frac{V'_{rms}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

$$\begin{aligned} V'_{rms} &= [V_{rms}^2 - V_{dc}^2]^{1/2} \\ &= \left[\left(\frac{V_m}{2} \right)^2 - \left(\frac{V_m}{\pi} \right)^2 \right]^{1/2} = 0.385V_m \end{aligned}$$

$$= \sqrt{\left(\frac{V_{rms}}{V_{dc}} \right)^2 - 1} = \sqrt{\left(\frac{V_m/2}{V_m/\pi} \right)^2 - 1}$$

\therefore Ripple factor = 1.21

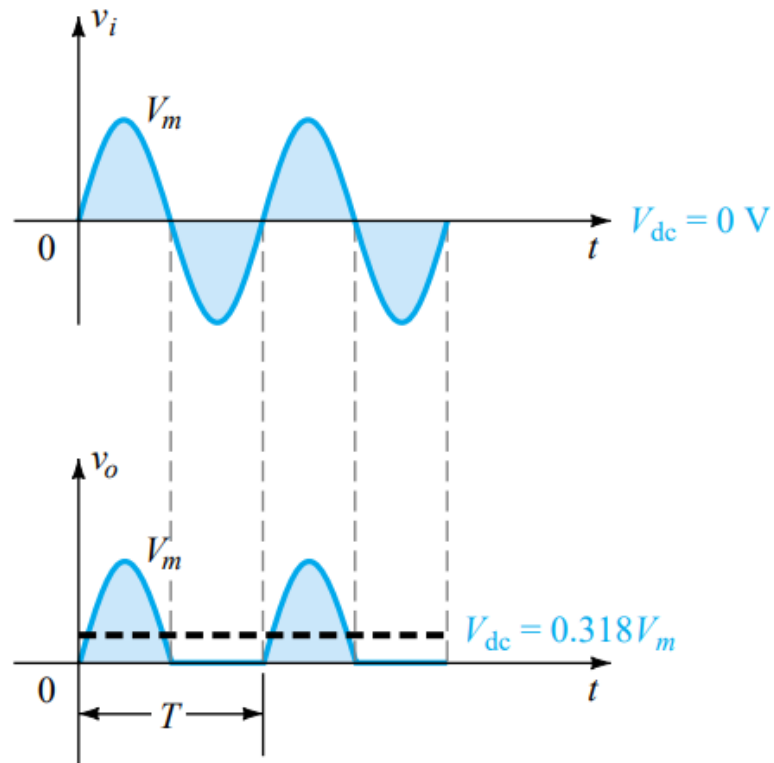
The time duration of 1 cycle of input waveform is T and the time duration of 1 cycle of output wave form is also T , hence $f_o = f_i$



ELECTRONIC PRINCIPLES AND DEVICES

Numerical on HWR

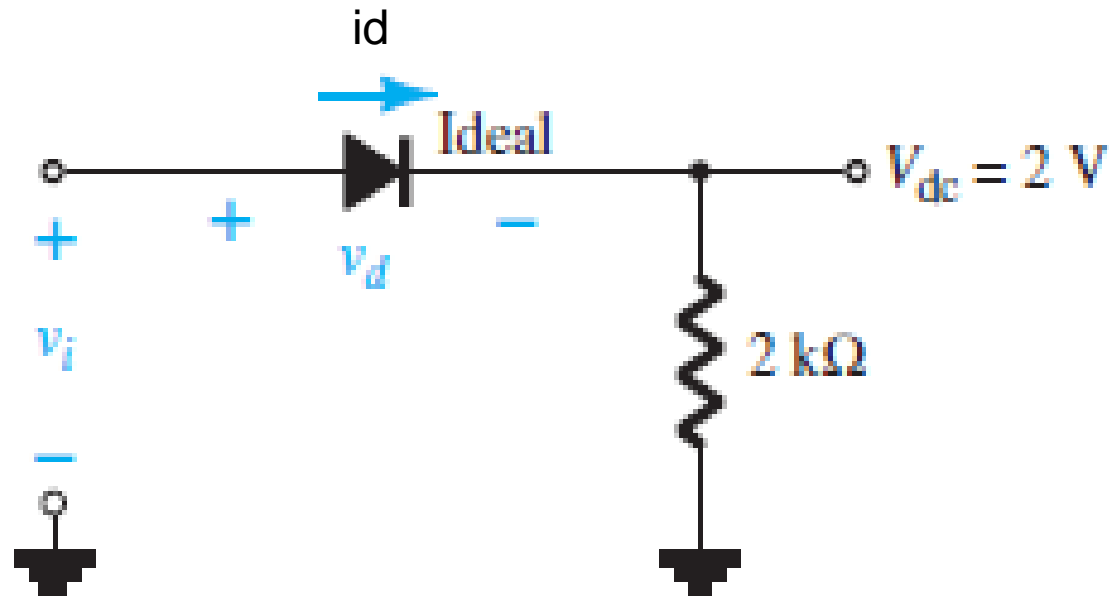1. a) Assuming an ideal diode, sketch V_i , V_d , and i_d for the half-wave rectifier. The input is a sinusoidal waveform with a frequency of 60 Hz




ELECTRONIC PRINCIPLES AND DEVICES




Numerical on HWR

Solution:
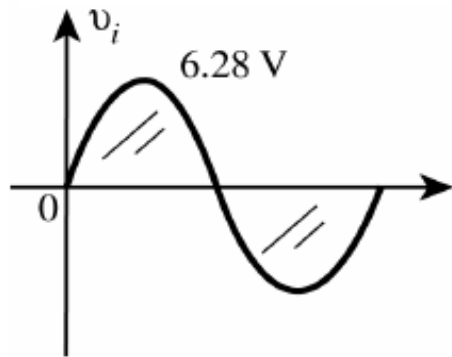
$$V_{dc} = 0.318 V_m \Rightarrow V_m = \frac{V_{dc}}{0.318} = \frac{2 \text{ V}}{0.318} = \mathbf{6.28 \text{ V}}$$



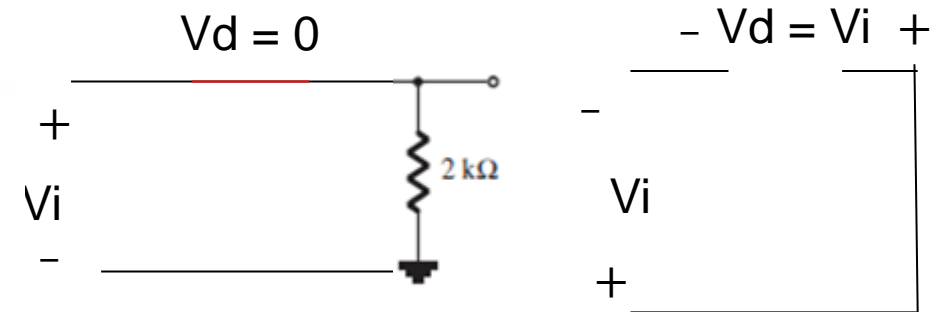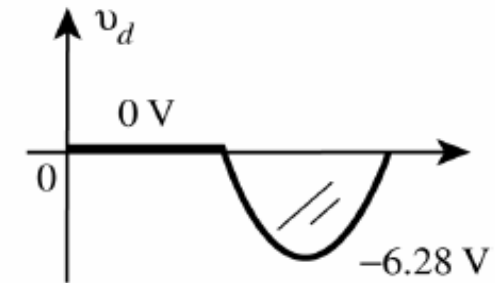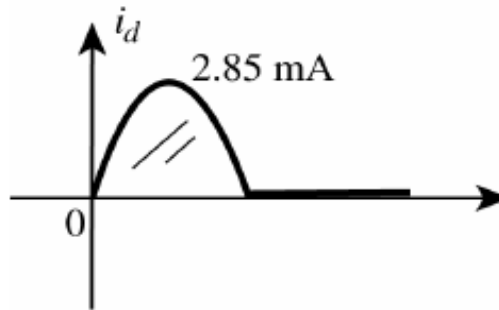
$$I_m = \frac{V_m}{R} = \frac{6.28 \text{ V}}{2.2 \text{ k}\Omega} = \mathbf{2.85 \text{ mA}}$$



ELECTRONIC PRINCIPLES AND DEVICES

Numerical on HWR

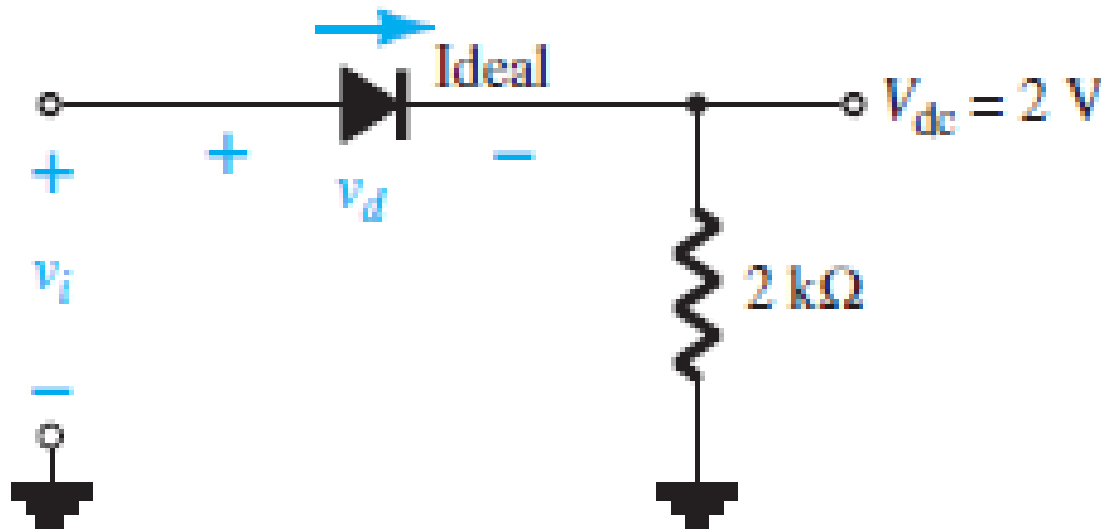1. b) Assuming a silicon diode ($V_k=0.7$ V), sketch v_i , v_d , and i_d for the half-wave rectifier. The input is a sinusoidal waveform with a frequency of 60 Hz



ELECTRONIC PRINCIPLES AND DEVICES


Numerical on HWR

Solution:

Using $V_{dc} \cong 0.318(V_m - V_k)$

$$2 \text{ V} = 0.318(V_m - 0.7 \text{ V})$$



Solving: $V_m = 6.98 \text{ V}$

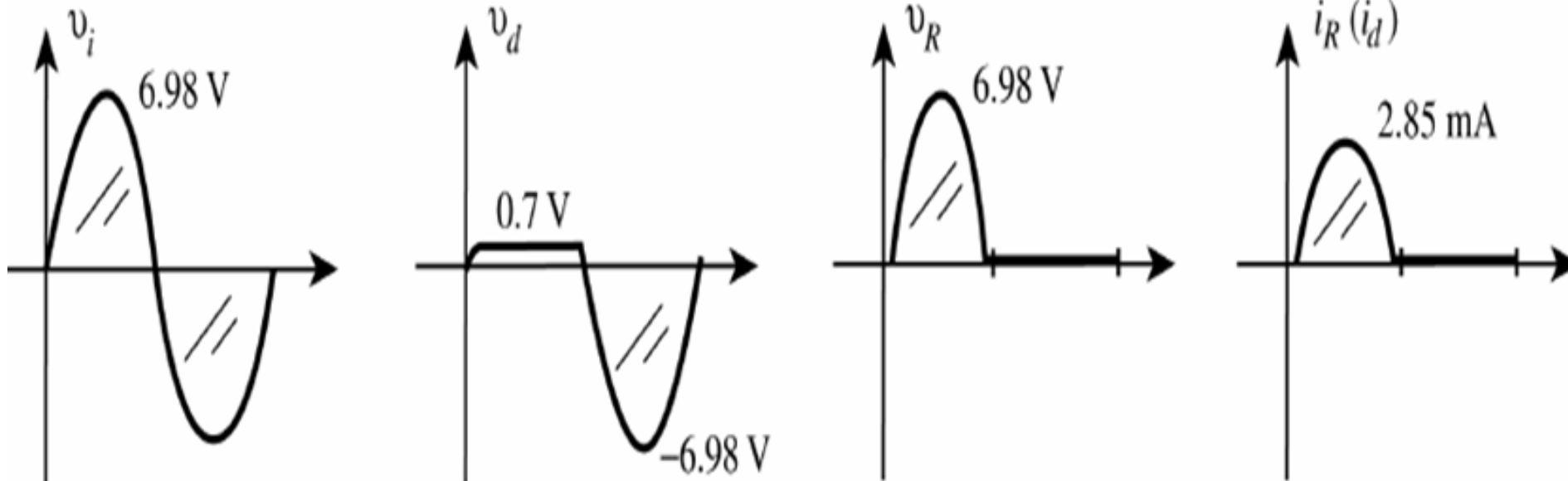

ELECTRONIC PRINCIPLES AND DEVICES

Numerical on HWR

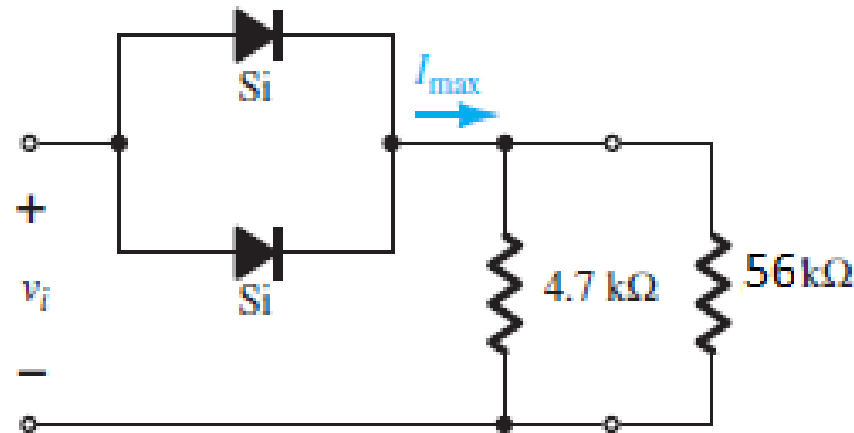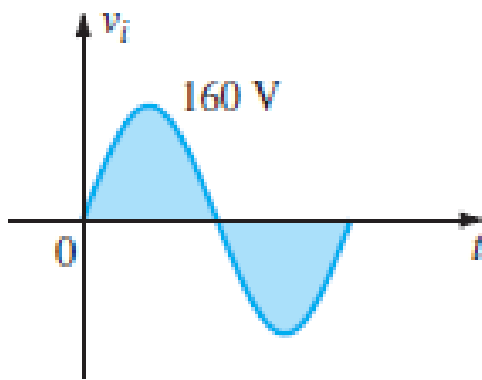2. (a) Given $P_{\max} = 14 \text{ mW}$ for each diode shown, determine the maximum current rating of each diode (using the approximate equivalent model).
- (b) Determine I_{\max} for $V_{\max} = 160 \text{ V}$.
- (c) Determine the current through each diode at V_{\max} using the results of part (b).
- (d) If only one diode were present, determine the diode current and compare it to the maximum rating.



ELECTRONIC PRINCIPLES AND DEVICES

Numerical on HWR

Solution:

(a) $P_{\max} = 14 \text{ mW} = (0.7 \text{ V})I_D$

$$I_D = \frac{14 \text{ mW}}{0.7 \text{ V}} = \mathbf{20 \text{ mA}}$$

(b) $4.7 \text{ k}\Omega \parallel 56 \text{ k}\Omega = 4.34 \text{ k}\Omega$


$$V_R = 160 \text{ V} - 0.7 \text{ V} = 159.3 \text{ V}$$

$$I_{\max} = \frac{159.3 \text{ V}}{4.34 \text{ k}\Omega} = \mathbf{36.71 \text{ mA}}$$

(c) $I_{\text{diode}} = \frac{I_{\max}}{2} = \frac{36.71 \text{ mA}}{2} = \mathbf{18.36 \text{ mA}} \quad I_D = 20 \text{ mA} > 18.36 \text{ mA}$

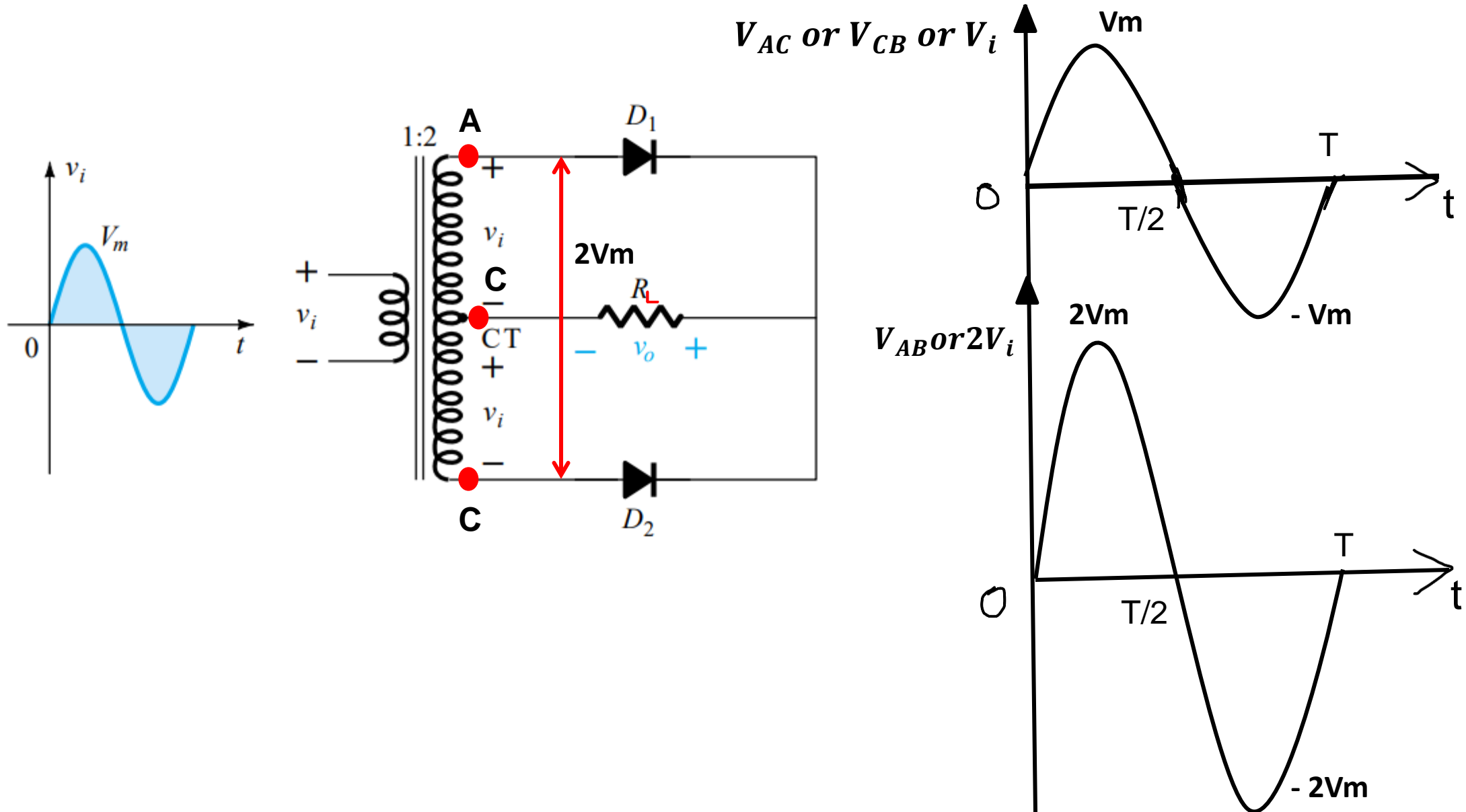
(d) $I_{\text{diode}} = 36.71 \text{ mA} \gg I_{\max} = 20 \text{ mA}$ **Total damage**

Full Wave Rectifier : Centre Tap (Ideal Diode)




Full Wave Rectifier : Centre Tap (Ideal Diode)

Positive Half Cycle:

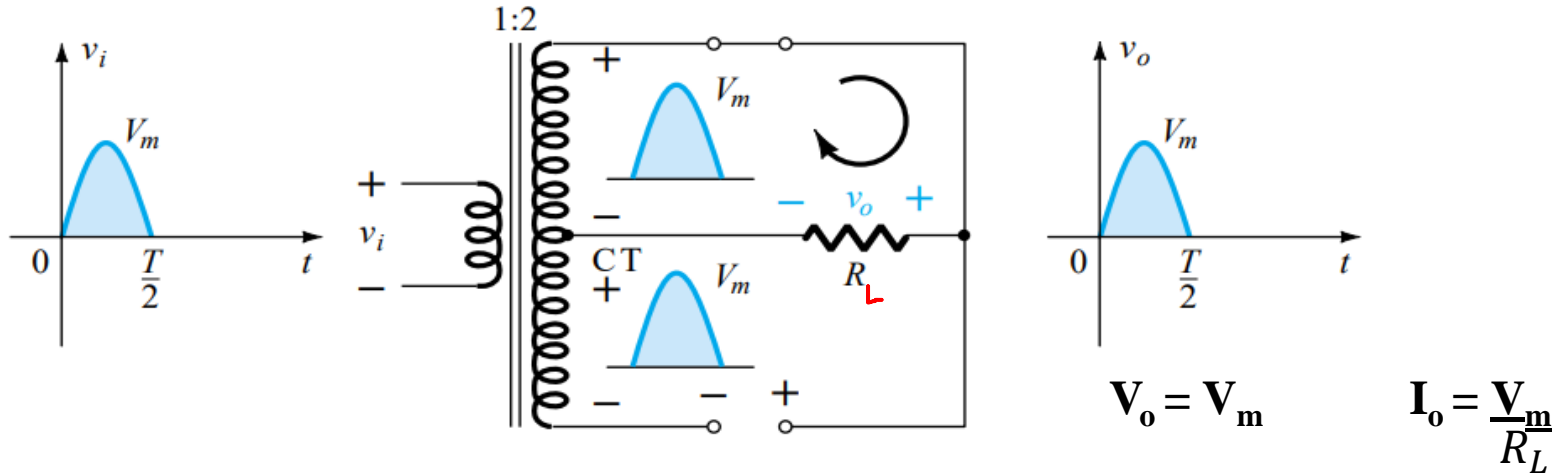


Negative Half Cycle:

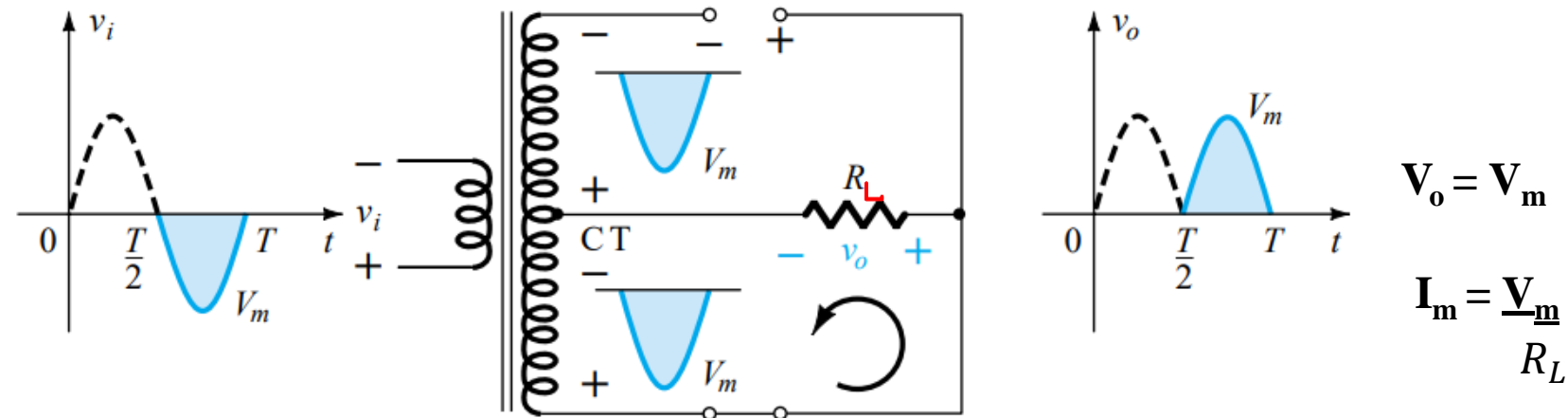

Full Wave Rectifier PIV - Centre Tap (Ideal Diode)
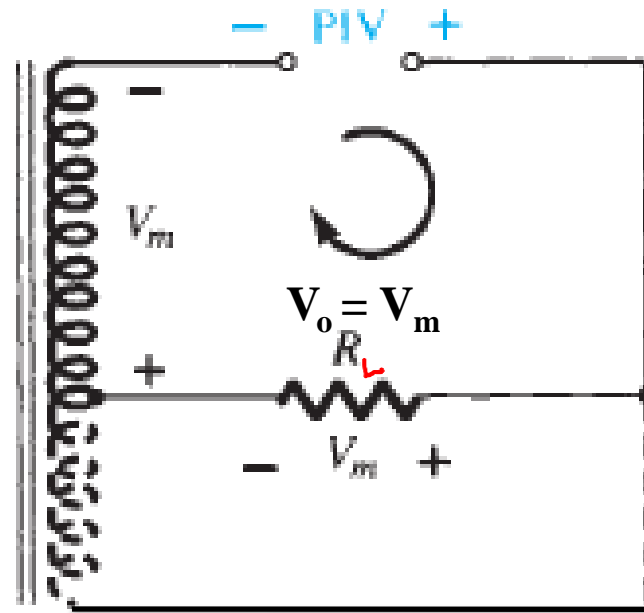
$$\begin{aligned} \text{PIV} &= V_{\text{secondary}} + V_R \\ &= V_m + V_m \end{aligned}$$




$$\text{PIV} \geq 2V_m$$

CT transformer, full-wave rectifier

Full Wave Rectifier : Centre Tap (Non Ideal Diode)

Negative Half Cycle:

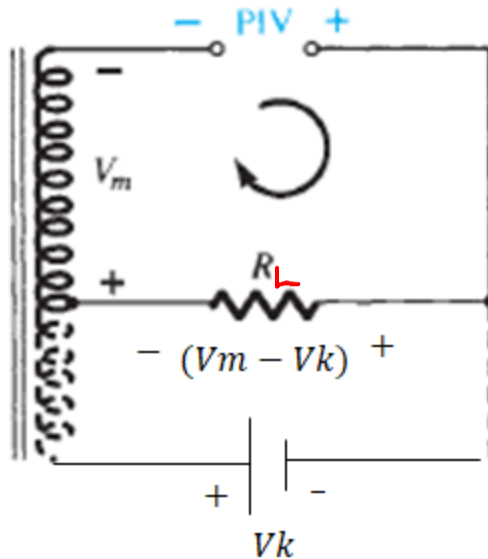

$$V_{o \max} = V_m - V_k$$

$$I_{o \max} = \frac{V_m - V_k}{R_L}$$



$$PIV - V_m + V_k - V_m = 0$$

$$PIV - 2V_m + V_k = 0$$


$$PIV = 2V_m - V_k$$

Non - Ideal diode: $PIV \geq 2V_m - V_k$

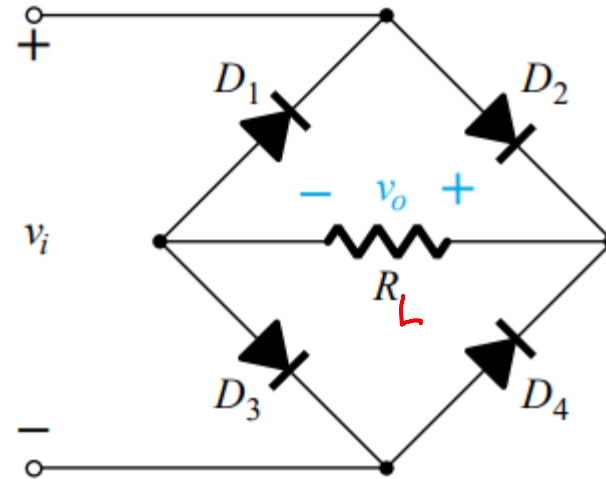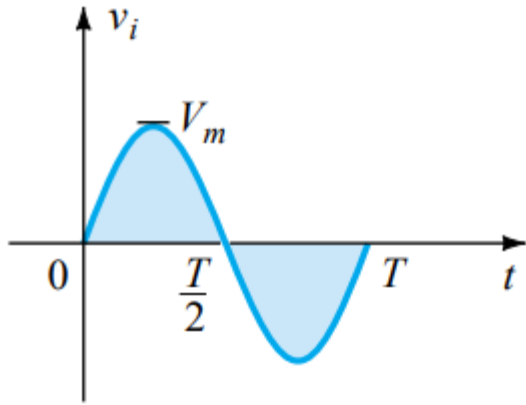Full Wave Rectifier: Bridge Rectifier (Ideal Diode)






Positive Half Cycle:

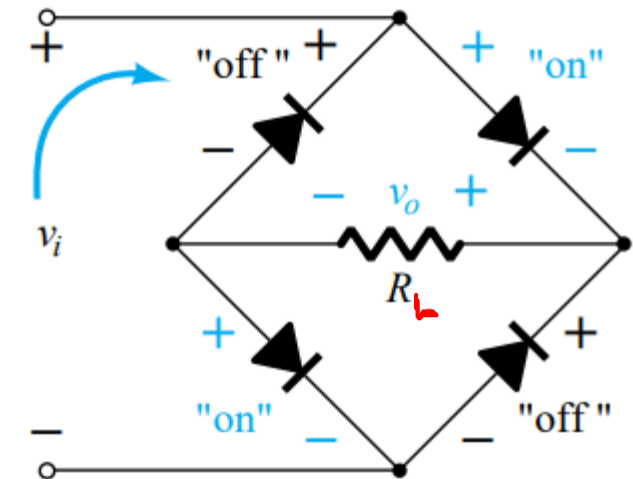

ELECTRONIC PRINCIPLES AND DEVICES

Full Wave Rectifier: Bridge Rectifier (Ideal Diode)


Positive Half Cycle:

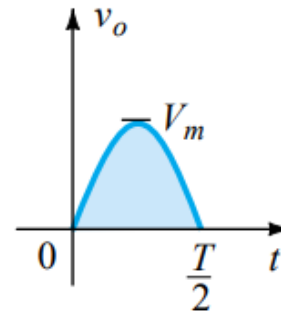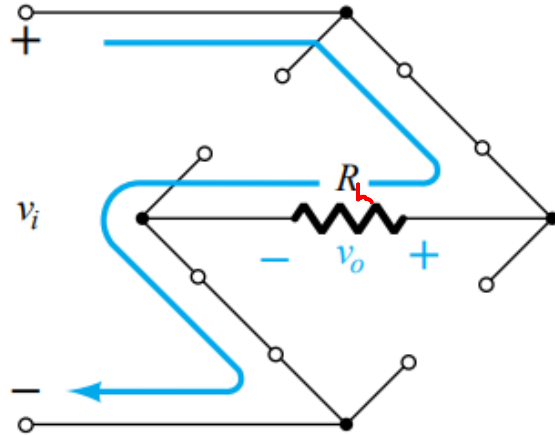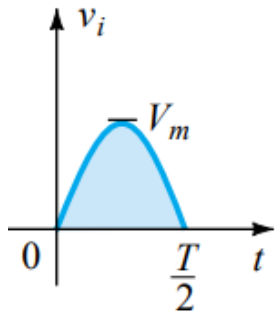




$$V_o = V_m$$

$$I_o = \frac{V_m}{R_L}$$


Input Waveform

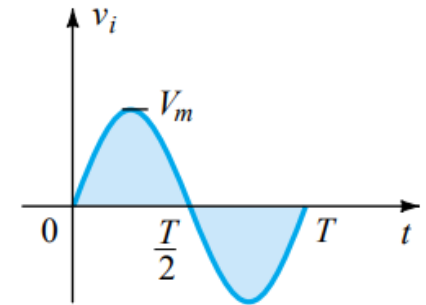

Negative Half Cycle:

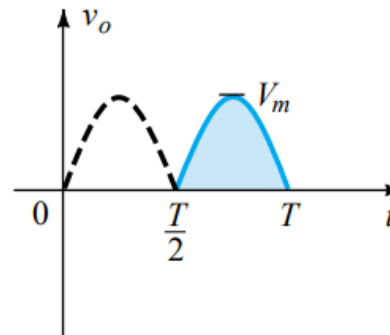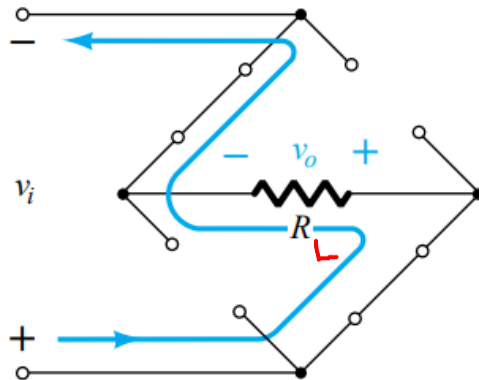
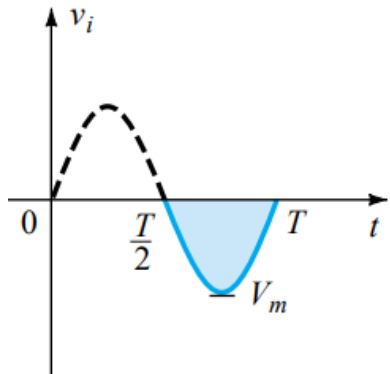


Output Waveform

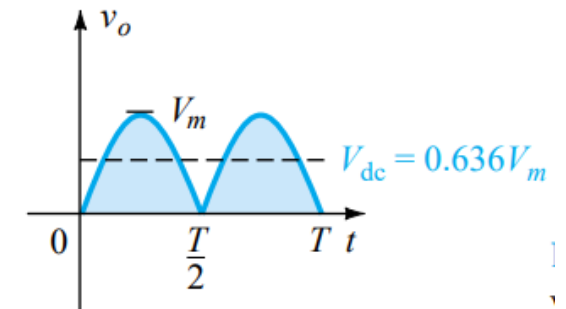

Full Wave Rectifier: Bridge Rectifier (Non Ideal Diode)

$$V_{dc} \cong 0.636(V_m - 2V_K)$$

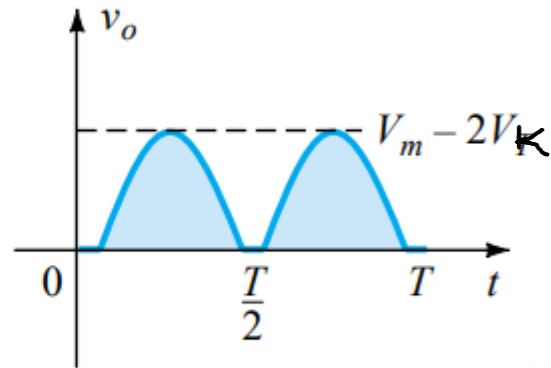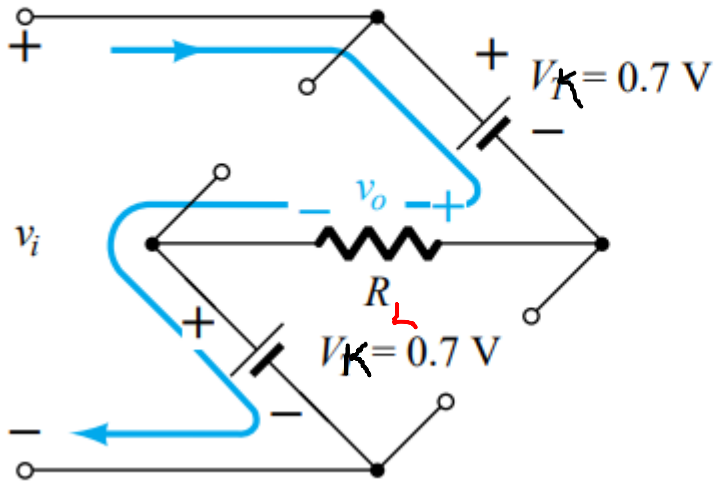

$$v_i - V_K - v_o - V_K = 0$$

$$v_o = v_i - 2V_K$$


$$V_{o_{\max}} = V_m - 2V_K$$

Full Wave Rectifier PIV : Bridge Rectifier (Ideal & Non-Ideal Diode)

Ideal diode: $\text{PIV} \geq V_m$ full-wave bridge rectifier

$$\text{PIV} - V_m = 0$$

$$\text{PIV} = V_m$$

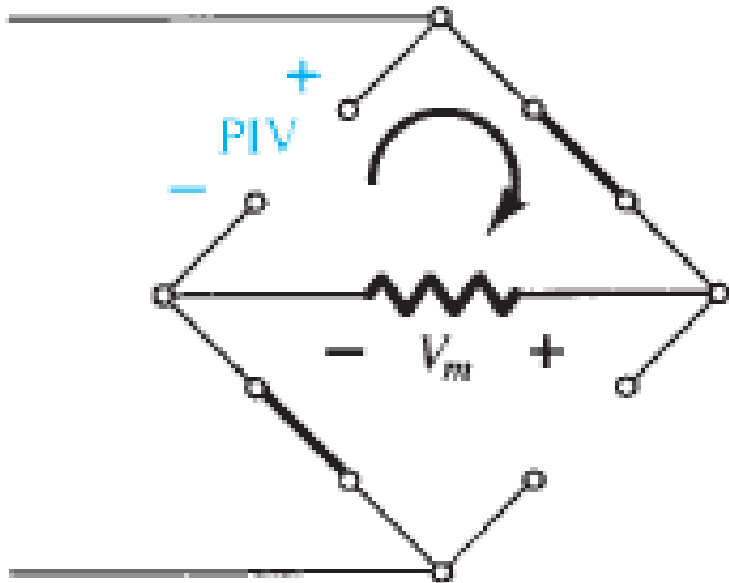


Non – Ideal diode: $\text{PIV} \geq V_m - V_k$

$$\text{PIV} - V_k - V_o = 0$$

$$\text{PIV} - V_k - V_m + 2V_k = 0$$

$$\text{PIV} + V_k - V_m = 0$$

$$\text{PIV} = V_m - V_k$$


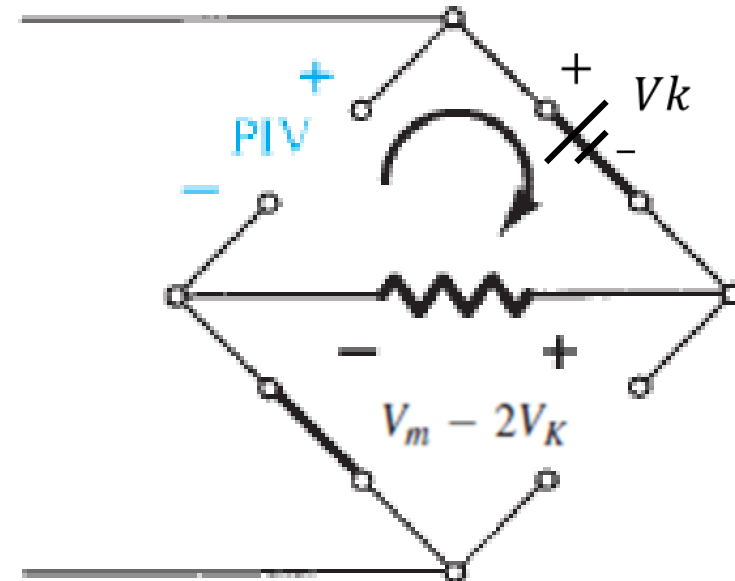


ELECTRONIC PRINCIPLES AND DEVICES

Determining Average voltage/ current for FWR (Ideal Diode)


$$\begin{aligned} V_{dc} &= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t \\ &= \frac{V_m}{\pi} [-\cos \omega t]_0^{\pi} \\ &= \frac{2V_m}{\pi} \end{aligned}$$
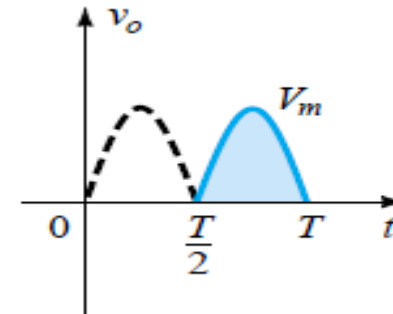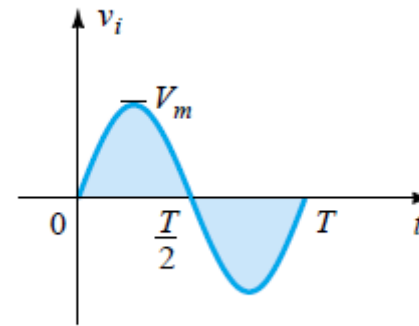
$$I_{dc} = \frac{V_{dc}}{R} = \frac{2V_m}{\pi R} = \frac{2I_m}{\pi}$$



Determining RMS voltage/ current for FWR (Ideal Diode)

$$\begin{aligned} V_{rms} &= \left[\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d\omega t \right]^{1/2} \\ &= \left[\frac{V_m^2}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]^{1/2} \\ &= \left[\frac{V_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) d\omega t \right]^{1/2} \\ &= \left[\frac{V_m^2}{2\pi} \left(\omega t \Big|_0^{\pi} - \frac{\sin 2\omega t}{2} \Big|_0^{\pi} \right) \right]^{1/2} = \left[\frac{V_m^2}{2\pi} (\pi - 0) \right]^{1/2} = \frac{V_m}{\sqrt{2}} \end{aligned}$$

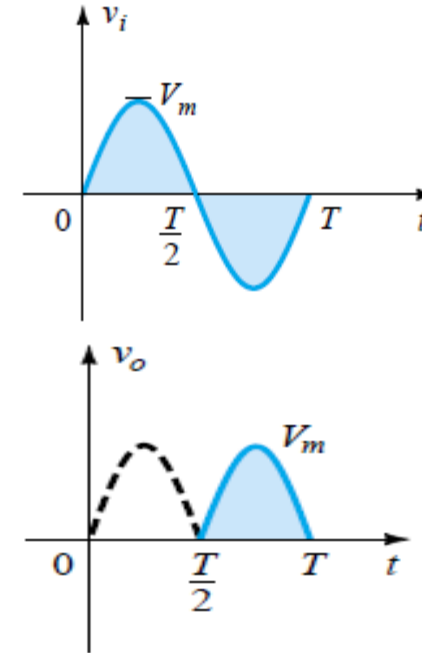

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{\sqrt{2}R} = \frac{I_m}{\sqrt{2}}$$

$$V_{dc} = \frac{2(V_m - V_k)}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{2(V_m - V_k)}{\pi R_L} = 2 \frac{I_m}{\pi} \quad \left(I_m = \frac{V_m - V_k}{R_L} \right)$$

$$V_{rms} = \frac{V_m - V_k}{\sqrt{2}}$$

$$I_{rms} = \frac{V_{rms}}{R_L} = \frac{V_m - V_k}{\sqrt{2} R_L} = \frac{I_m}{\sqrt{2}} \quad \left(I_m = \frac{V_m - V_k}{R_L} \right)$$

Average & RMS voltage/Current for Bridge Rectifier- Non ideal Diode

$$V_{dc} = \frac{2(V_m - 2V_k)}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{2(V_m - 2V_k)}{\pi R_L} = 2 \frac{I_m}{\pi} \quad \left(I_m = \frac{V_m - 2V_k}{R_L} \right)$$

$$V_{rms} = \frac{V_m - 2V_k}{\sqrt{2}}$$

$$I_{rms} = \frac{V_{rms}}{R_L} = \frac{V_m - 2V_k}{\sqrt{2} R_L} = \frac{I_m}{\sqrt{2}} \quad \left(I_m = \frac{V_m - 2V_k}{R_L} \right)$$

Ripple factor of FWR

Ripple Factor is a measure of purity of the dc output of a rectifier and can be defined as

$$r = \frac{\text{rms value of the ac component of the output}}{\text{average or dc value of the output}}$$


$$\text{Ripple Factor } (\gamma_{\text{FWR}}) = \frac{V'_{rms}}{V_{dc}} =$$

$$= \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{V_m/\sqrt{2}}{2V_m/\pi}\right)^2 - 1}$$

$$V_{rms}^I = \sqrt{V_{rms}^2 - V_{dc}^2}$$
$$= \sqrt{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2} = 0.307 V_m$$

$$\therefore \text{Ripple factor} = 0.48$$

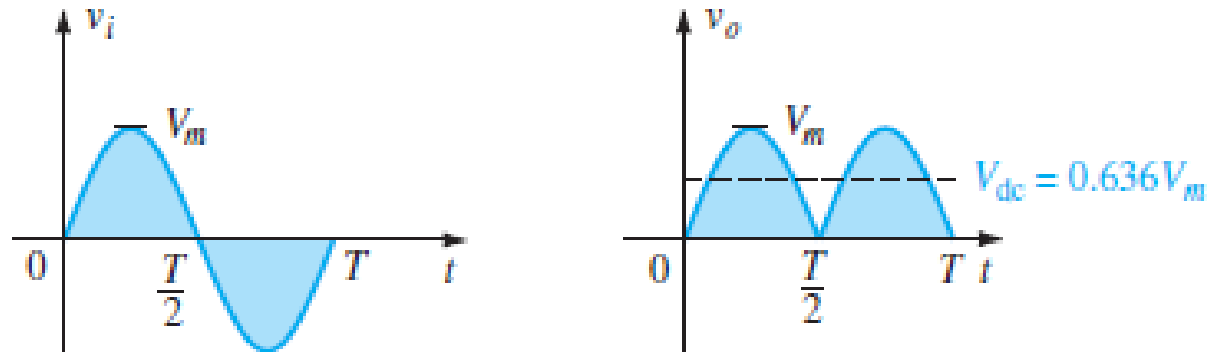The time duration of 1 cycle of input waveform is T and the time duration of 1 cycle of output wave form is $T/2$, hence $f_o = 2 f_i$



ELECTRONIC PRINCIPLES AND DEVICES

Comparison Table for HWR & FWR

Measure	HWR Ideal	HWR Practical	CT-Ideal	CT-Practical	Bridge- Ideal	Bridge-Practical
I_{dc}	$\frac{I_m}{\pi}$	$\frac{I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$
V_{dc}	$\frac{V_m}{\pi}$	$\frac{V_m - V_k}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2(V_m - V_k)}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2(V_m - 2V_k)}{\pi}$
I_{rms}	$\frac{I_m}{2}$	$\frac{I_m}{2}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$
V_{rms}	$\frac{V_m}{2}$	$\frac{V_m - V_k}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m - V_k}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m - 2V_k}{\sqrt{2}}$
PIV	V_m	V_m	$2V_m$	$2V_m - V_k$	V_m	$V_m - V_k$


ELECTRONIC PRINCIPLES AND DEVICES

Differences between Centre Tap & Bridge FWR

Sl No.	Bridge-FWR	CT- FWR
1	Lesser PIV	Comparatively higher PIV
2	Centre tap transformer not required	Centre tap transformer required
3	Uniform input for both half cycles	Difficult to balance both the half cycles due to CT
4	4 diodes are required	2 diodes are required
5	More voltage drop due to two diodes in the path	Comparatively less voltage drop due to only one diode in the path

Numerical on Full Wave Rectifier: Bridge Rectifier




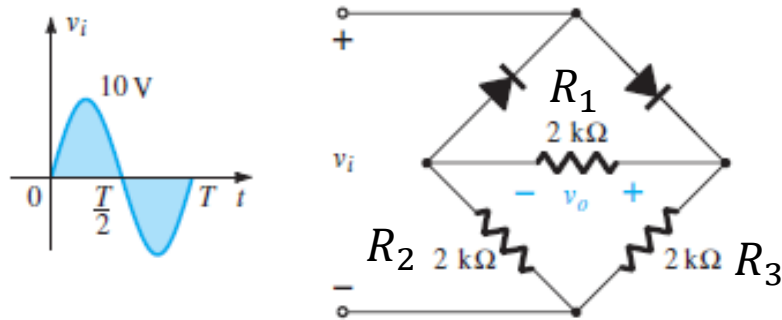
1. Determine the output waveform for the network and calculate the output dc level and the required PIV of each diode.







Solution:

Voltage Divider Rule : $\frac{V_i R_1}{R_1 + R_2} = V_o$

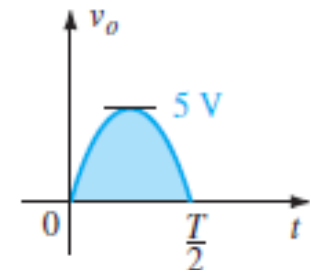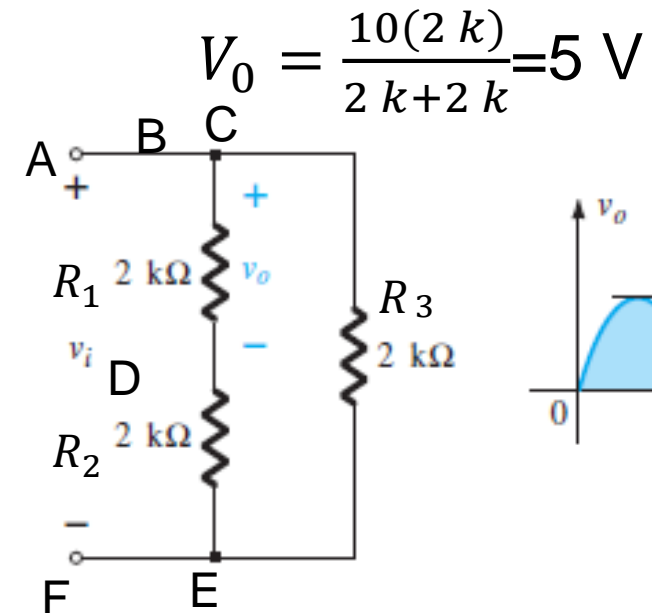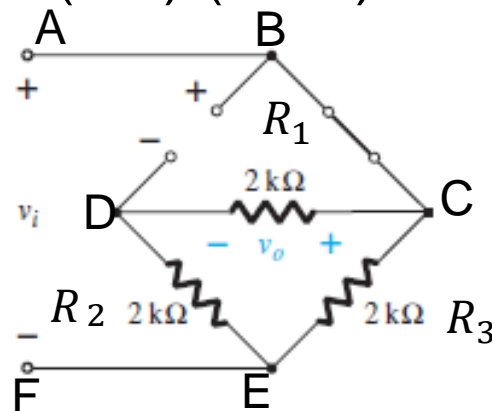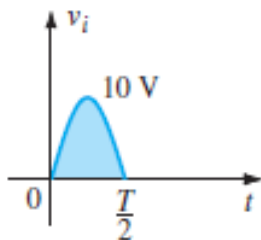$V_{o\max} = (2/4) V_{i\max} = (2/4) (10 \text{ V}) = 5 \text{ V}$



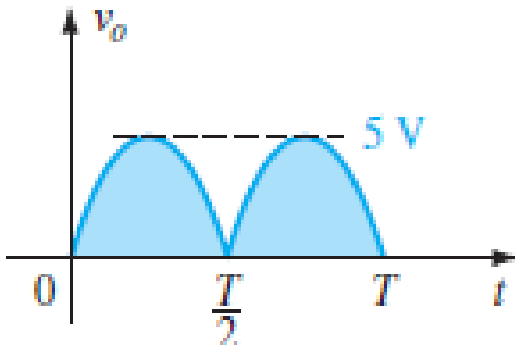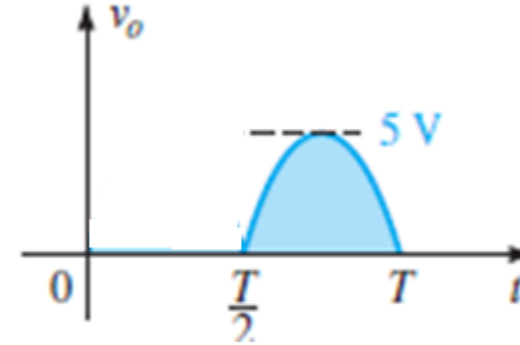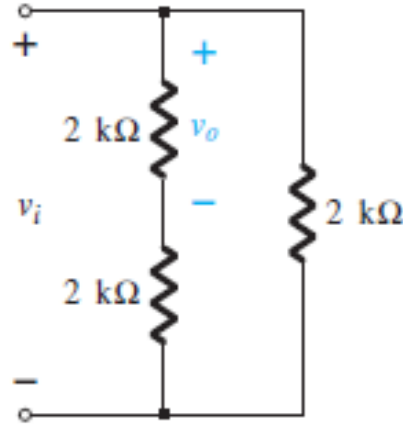
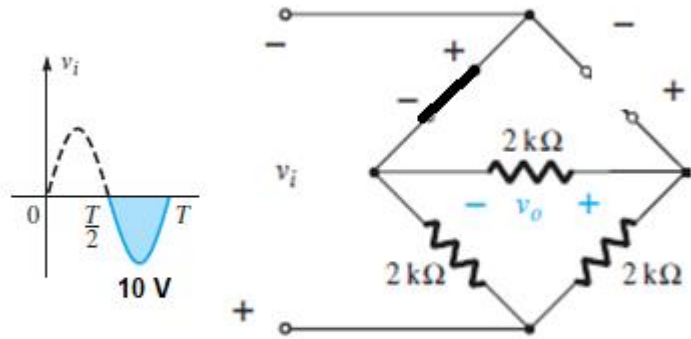
Numerical on Full Wave Rectifier: Bridge Rectifier



$$V_{dc} = 0.636(5\text{ V}) = 3.18\text{ V}$$



Numerical on Full Wave Rectifier: Bridge Rectifier

Sketch v_o for the network

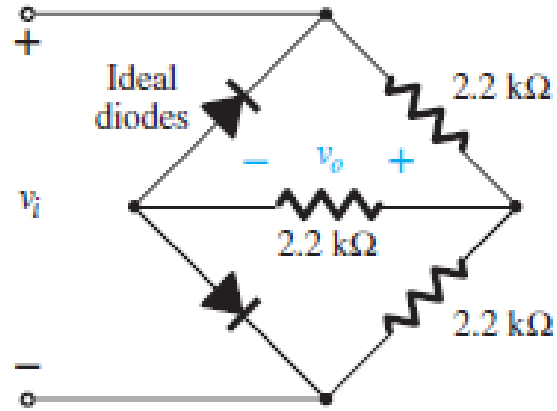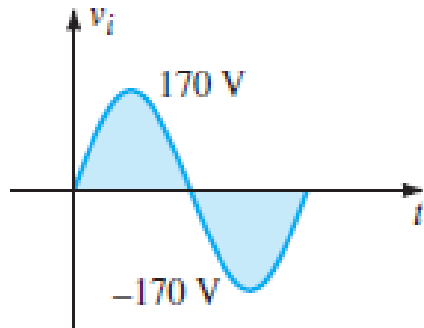

Numerical on Full Wave Rectifier: Bridge Rectifier

Sketch v_o for the network

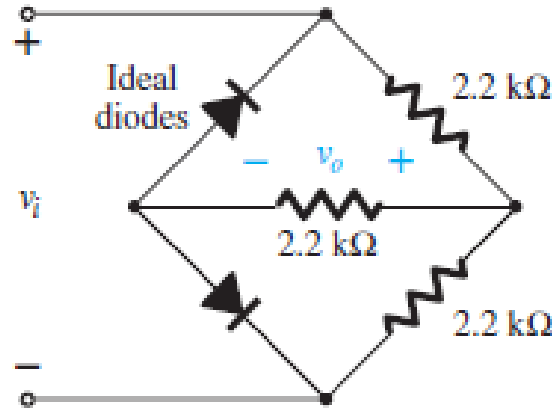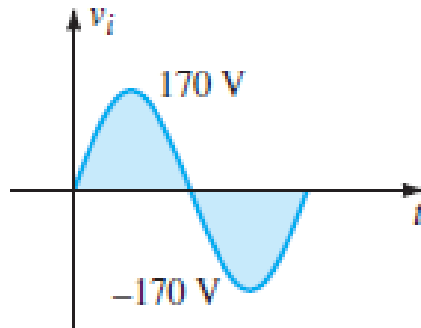

Positive pulse of v_i :

Top left diode “off”, bottom left diode “on”

$$2.2 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.1 \text{ k}\Omega$$

$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega (170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$

Negative pulse of v_i :

Top left diode “on”, bottom left diode “off”


$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega (170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$

$$V_{\text{dc}} = 0.636(56.67 \text{ V}) = \mathbf{36.04 \text{ V}}$$

ELECTRONIC PRINCIPLES AND DEVICES

Full Wave Rectifier

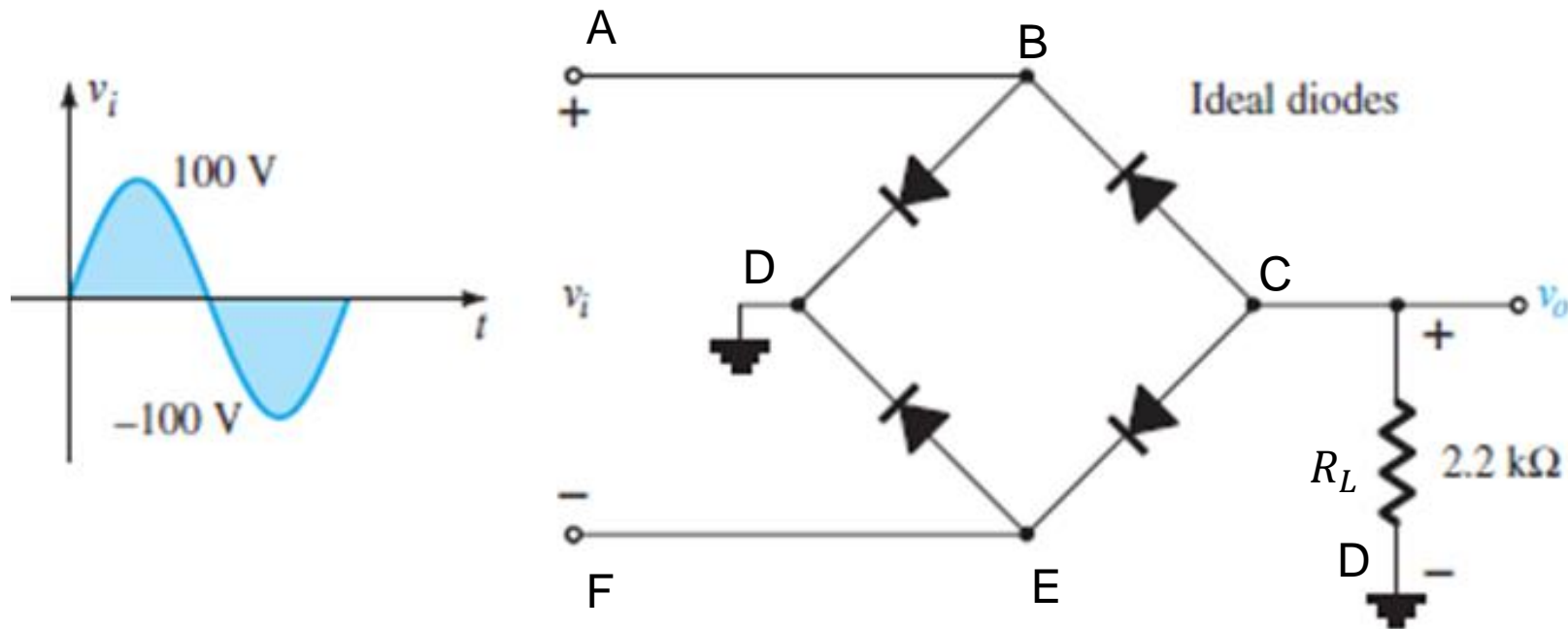3. Determine V_o and the required PIV rating of each diode for the configuration of Fig. In addition, determine the maximum current through each diode.



For positive cycle


Path : ABDCEF

Applying KVL

$$V_i + V_o = 0 ; V_o = -V_i$$

For Negative cycle:


Path : FEDCBA

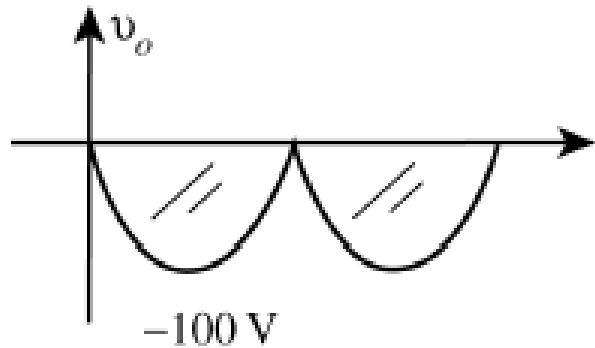

$$\text{PIV} = 100 \text{ V}$$


$$I_{\max} = \frac{100 \text{ V}}{2.2 \text{ k}\Omega} = 45.45 \text{ mA}$$

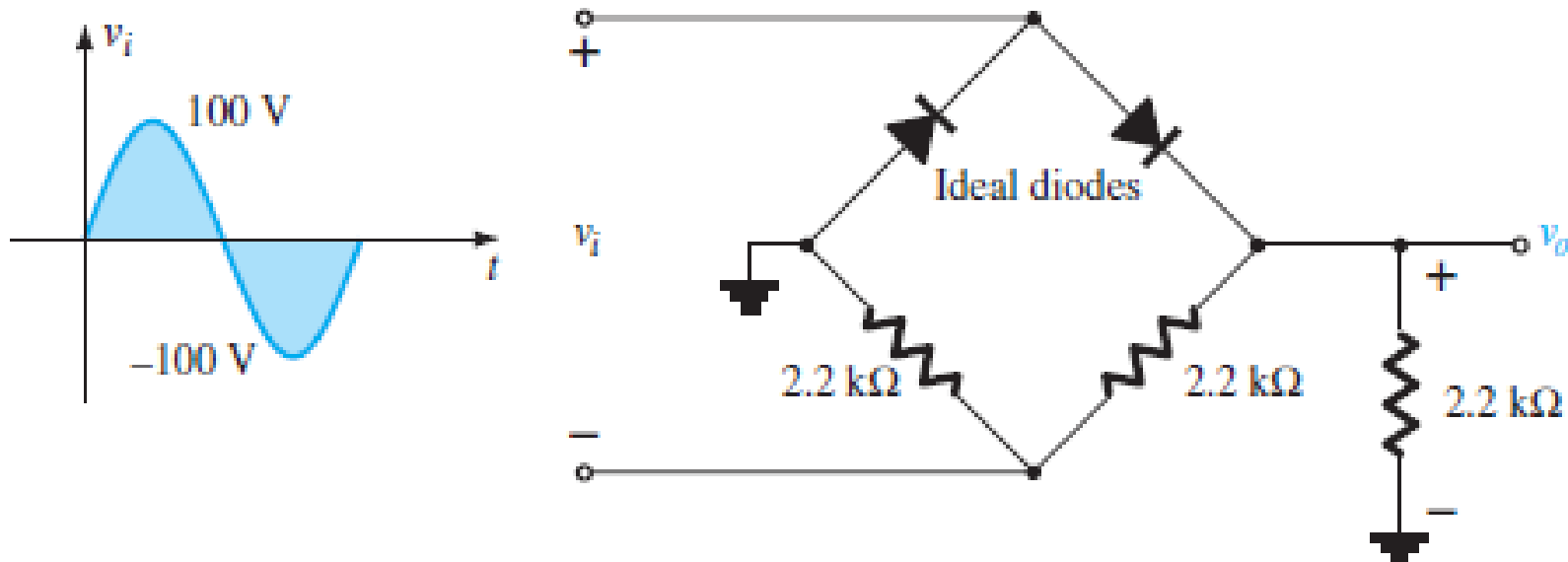4. Sketch V_o for the network of Fig. and determine the dc voltage available.



Positive half-cycle of v_i :

Network redrawn:

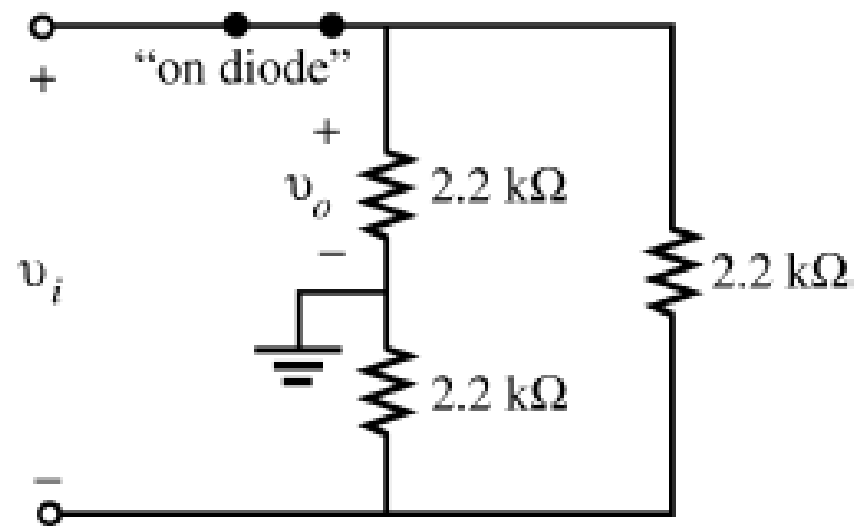


Voltage-divider rule:

$$\begin{aligned} V_{o_{\max}} &= \frac{2.2 \text{ k}\Omega (V_{i_{\max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2} (V_{i_{\max}}) \\ &= \frac{1}{2} (100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$

ELECTRONIC PRINCIPLES AND DEVICES


Numerical on Full Wave Rectifier: Bridge Rectifier

Negative half-cycle of v_i :

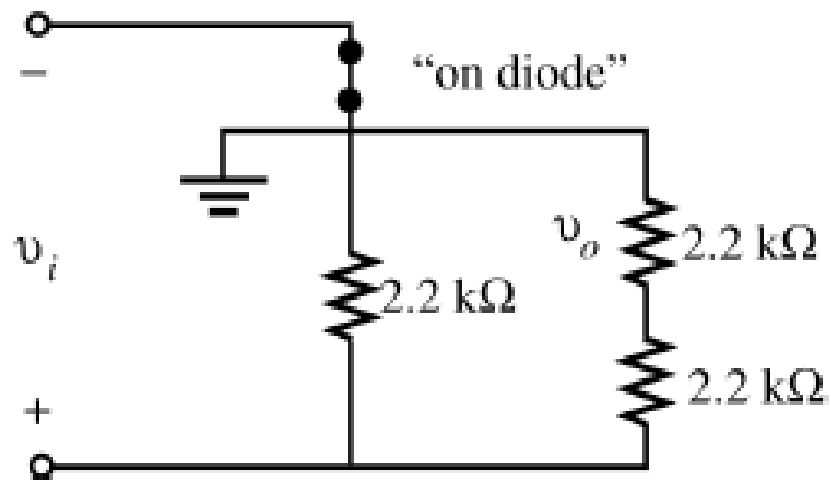


Voltage-divider rule:
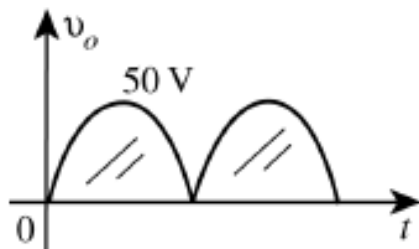
$$\begin{aligned} V_{o_{\max}} &= \frac{2.2 \text{ k}\Omega (V_{i_{\max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2} (V_{i_{\max}}) \\ &= \frac{1}{2} (100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$




$$\begin{aligned} V_{\text{dc}} &= 0.636 V_m = 0.636 (50 \text{ V}) \\ &= 31.8 \text{ V} \end{aligned}$$

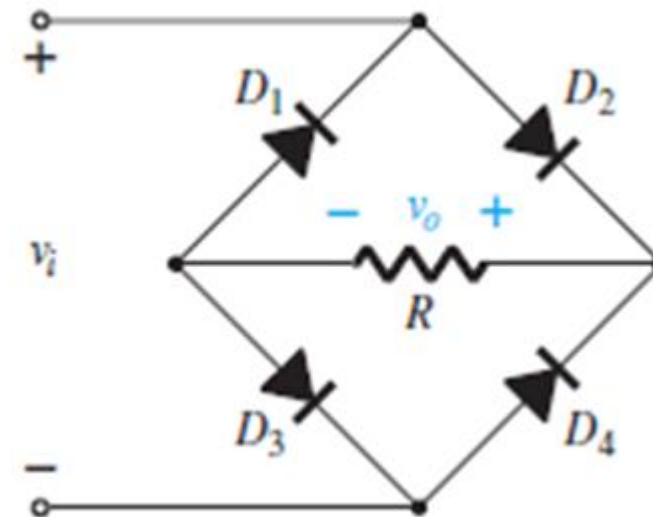5. A full-wave bridge rectifier with a 120-V rms sinusoidal input has a load resistor of 1 k Ω .
- (a) If silicon diodes are employed, what is the dc voltage available at the load?
 - (b) Determine the required PIV rating of each diode.
 - (c) Find the maximum current through each diode during conduction.
 - (d) What is the required power rating of each diode?



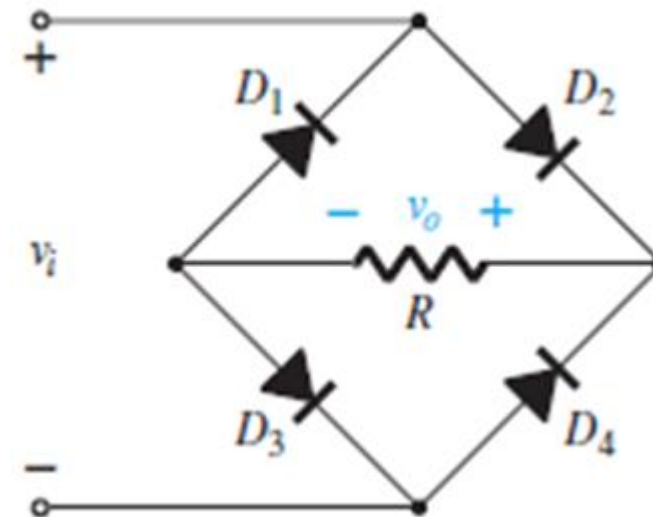5. A full-wave bridge rectifier with a 120-V rms sinusoidal input has a load resistor of 1 k Ω .
- (a) If silicon diodes are employed, what is the dc voltage available at the load?
 - (b) Determine the required PIV rating of each diode.
 - (c) Find the maximum current through each diode during conduction.
 - (d) What is the required power rating of each diode?



$$(a) \quad V_m = \sqrt{2} (120 \text{ V}) = 169.7 \text{ V}$$

$$V_{L_m} = V_{i_m} - 2V_D$$

$$= 169.7 \text{ V} - 2(0.7 \text{ V}) = 169.7 \text{ V} - 1.4 \text{ V}$$

$$= 168.3 \text{ V}$$

$$V_{dc} = 0.636(168.3 \text{ V}) = \mathbf{107.04 \text{ V}}$$

$$(b) \quad \text{PIV} : V_m - V_k = 169.7 - 0.7 \quad = \mathbf{169 \text{ V}}$$

$$(c) \quad I_D(\text{max}) = \frac{V_{L_m}}{R_L} = \frac{168.3 \text{ V}}{1 \text{ k}\Omega} = 168.3 \text{ mA}$$

$$\begin{aligned}(d) \quad P_{\text{max}} &= V_D I_D = (0.7 \text{ V}) I_{\text{max}} \\ &= (0.7 \text{ V})(168.3 \text{ mA}) \\ &= 117.81 \text{ mW}\end{aligned}$$

6. The input to a bridge rectifier is given through a 10 : 1 transformer from a supply of $230 \sin 314 t$. If $R_L = 500 \Omega$. Determine

DC load voltage

RMS load voltage

PIV across diodes

DC power delivered to the load

Frequency of output waveform

The primary voltage of transformer, $V_1 = 230 \sin 314 t$

Transformer turns ration, $\frac{N_1}{N_2} = \frac{10}{1}$

The secondary voltage of transformer, $V_2 = \frac{N_2}{N_1} V_1 = \frac{1}{10} 230 \sin 314 t$

$$V_2 = 23 \sin 314 t$$

$$V_2 = V_m \sin \omega t = 23 \sin 314 t$$

Therefore, $V_m = 23 V$

$$\text{DC load voltage, } V_{dc} = \frac{2 V_m}{\pi} = \frac{2 \times 23}{\pi} = 14.64 \text{ V}$$

$$\text{RMS load voltage, } V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{23}{\sqrt{2}} = 16.26$$

$$\text{PIV across diodes, } PIV \geq V_m \geq 23 \text{ V}$$

$$\text{DC power delivered to the load, } P_{dc} = I_{dc}^2 \times R_L = \frac{V_{dc}^2}{R_L} = 0.428 \text{ W}$$

$$\text{Frequency of output waveform, } f_o = 2f_i = 100 \text{ Hz}$$


7. In a two diode FWR using Si diodes, the RMS voltage across each half of the transformer secondary is 100V. The load resistance is $975\ \Omega$ Find (i) Average current (ii) Average output voltage (iii) PIV of diode.

Ans: $V_{dc} = 89.57V$, $I_{dc} = 91.8mA$ and $PIV = 282.1V$.

8. A Bridge rectifier with ideal diodes has an ac source of RMS value 220 V, 50Hz connected to the primary of transformer. If the load resistance is 200Ω and turns ratio of transformer is 4:1, find the dc output voltage, dc output current and output frequency.

Ans: $V_{dc} = 49.6V$, $I_{dc} = 248mA$ and $f_o = 100Hz$.

Shunt Capacitor Filter

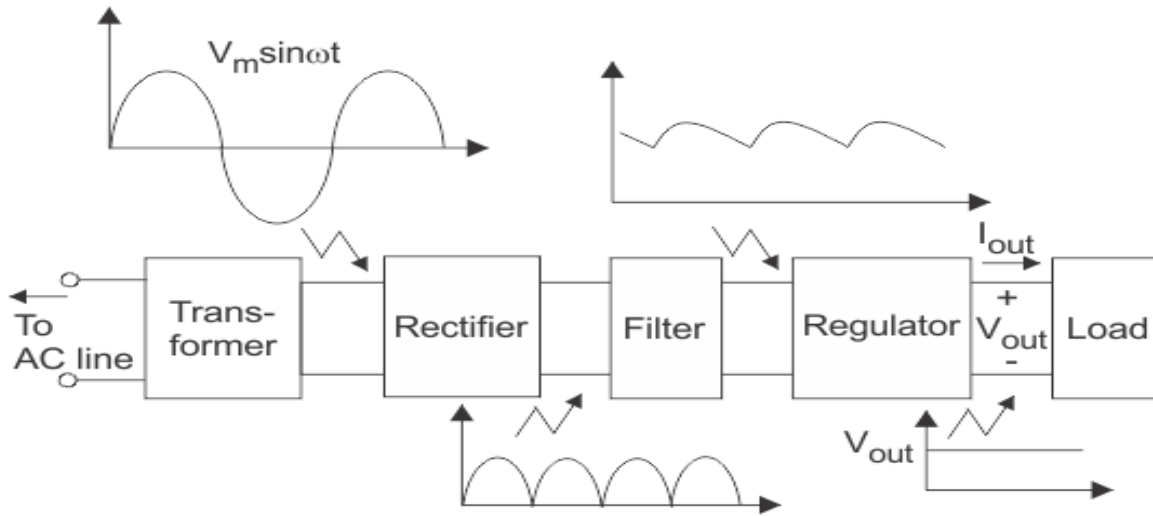


Components of typical linear power supply

Filter is a circuit which converts pulsating DC to smooth DC. Since the reactance of capacitor and inductor depends on frequency, by connecting a capacitor in parallel with the load or by connecting an inductor in series with the load, the ac ripple present at the output of a rectifier can be reduced.

ELECTRONIC PRINCIPLES AND DEVICES

FWR with Shunt Capacitor Filter

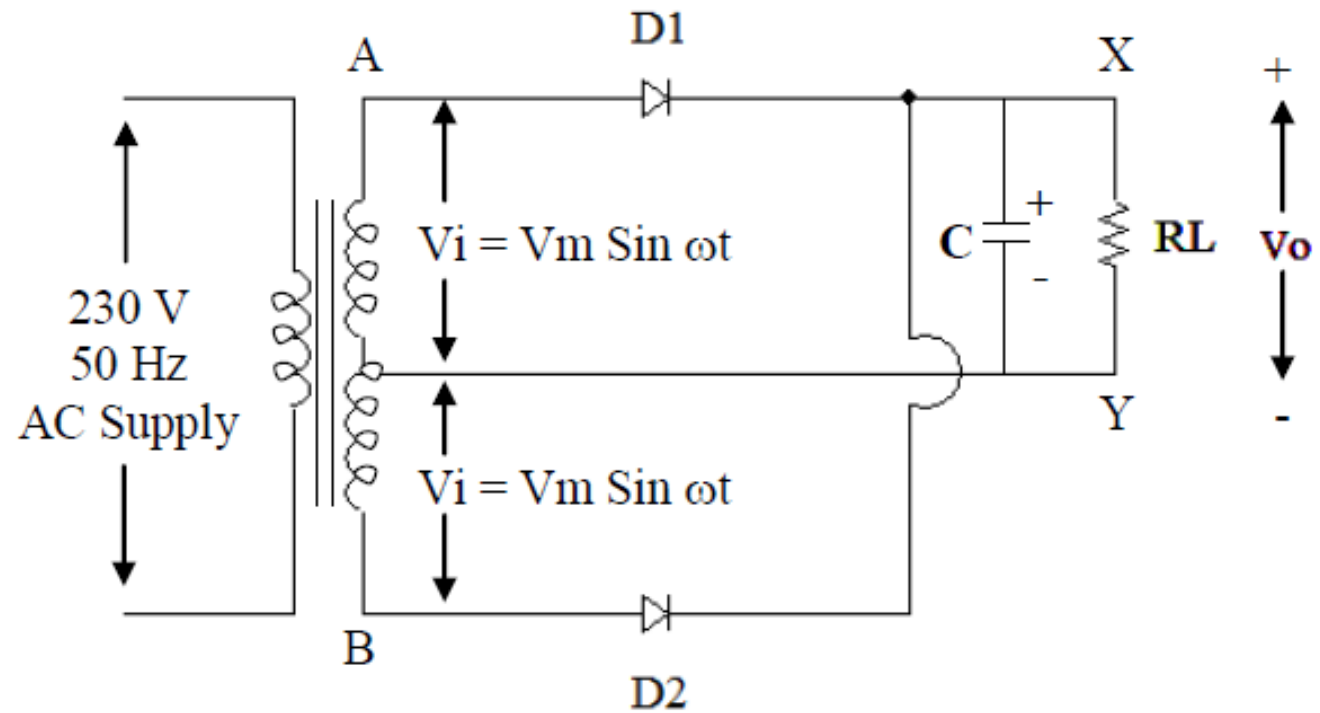


Working

During positive half cycle the diode D1 is forward biased in centre tap full wave rectifier and diode D1 and D2 are forward biased in bridge rectifier. Hence the capacitor C will charge from 0 V towards the peak value of input V_m . When input voltage V_i reaches V_m the charge on capacitor will also be equal to V_m , hence the diodes will turn off (since both anode and cathode of diodes will be at same potential). Now the capacitor starts discharging through the load R_L , if the load is very light (load resistance is very high and load current is low) the capacitor will discharge by a small amount, by that time next half cycle charges the capacitor back to V_m . Thus the output voltage remains almost constant.

ELECTRONIC PRINCIPLES AND DEVICES

Shunt Capacitor Filter

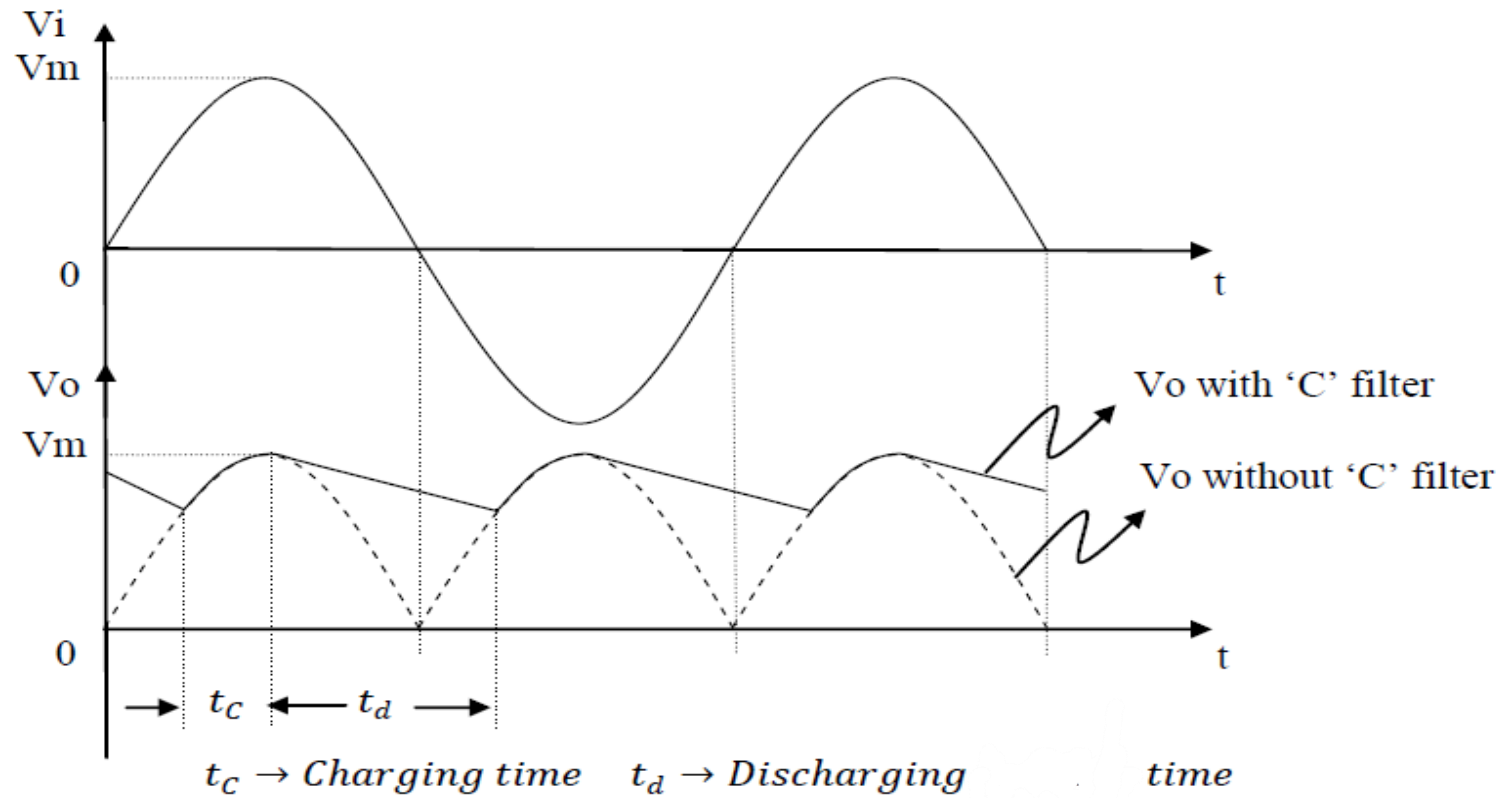

Expression for ripple factor

$$\gamma = \frac{1}{4\sqrt{3}fCR_L}$$

$f \rightarrow$ Frequency of input AC signal
 $C \rightarrow$ Filter capacitor used
 $R_L \rightarrow$ Load resistance

$$\gamma \propto \frac{1}{f} \quad \frac{1}{C} \quad \frac{1}{R_L}$$



Since ripple is inversely proportional to frequency, capacitor and load resistance, the ripple can be minimized by using high value of C. (R_L and f are not in designer's hand)

$$\gamma = \frac{V_{r(rms)}}{V_{dc}}, V_{r(rms)} = \frac{I_{DC}}{4\sqrt{3}fc},$$

$$V_{dc} = V_m - \frac{I_{DC}}{4fc}$$

ELECTRONIC PRINCIPLES AND DEVICES

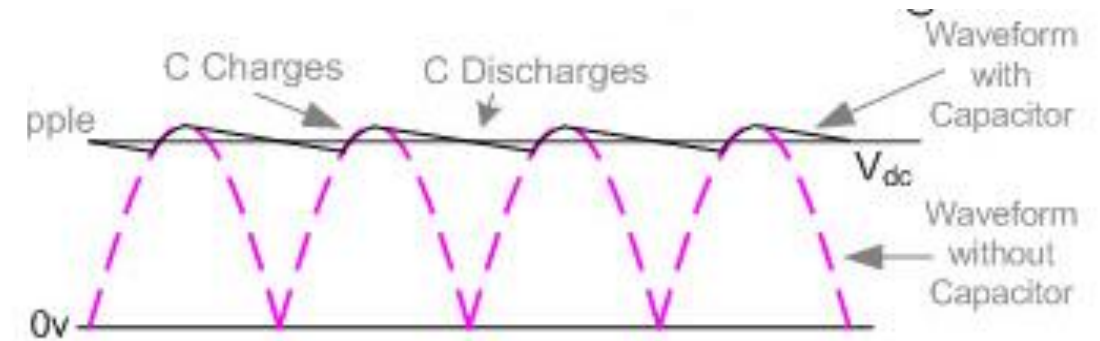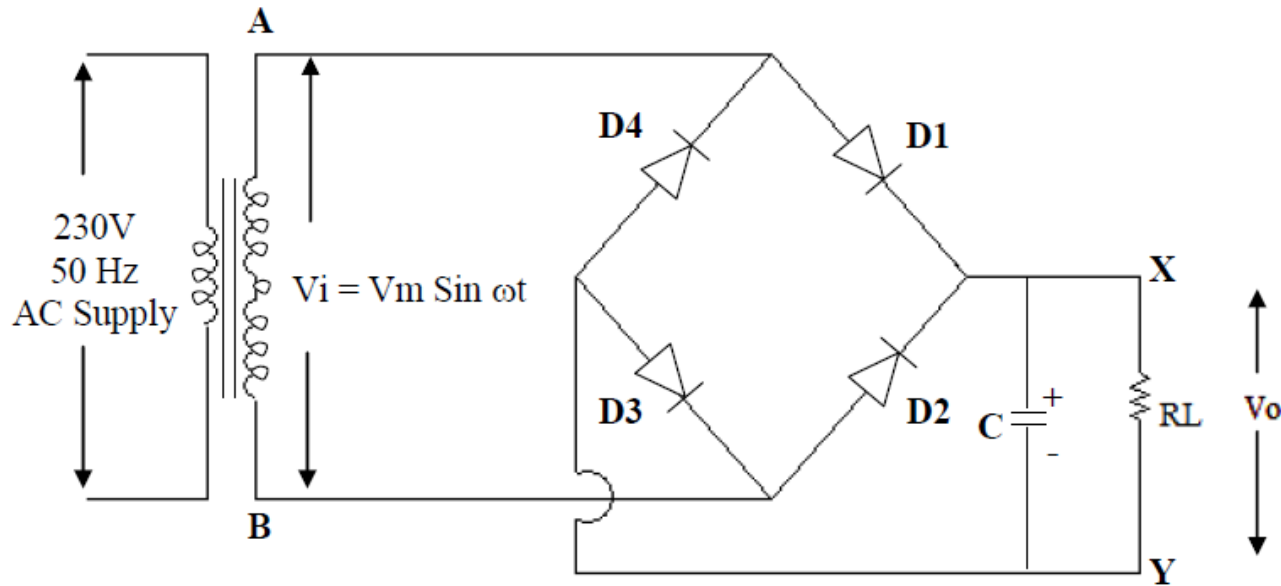Shunt Capacitor Filter for Bridge Rectifier





- AC components fluctuate with respect to time while the DC components remain constant with respect to time
- So the AC components present in the pulsating DC is an unwanted signal

ELECTRONIC PRINCIPLES AND DEVICES

Shunt Capacitor Filter for Half – Wave Rectifier

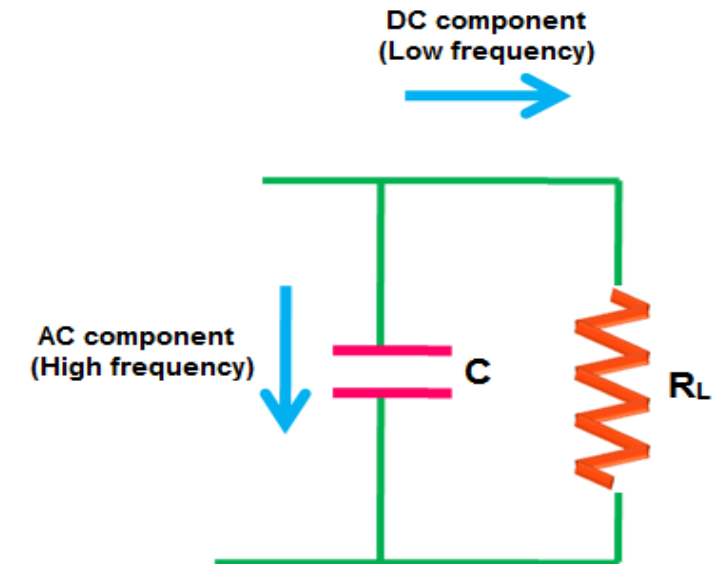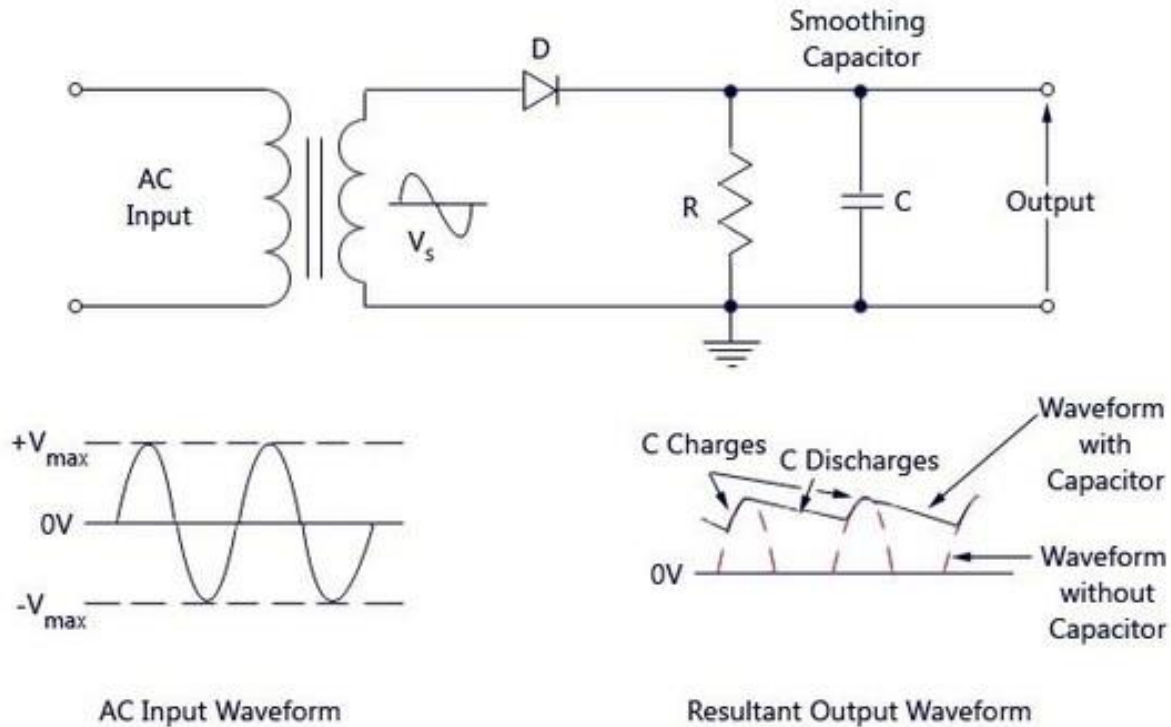Capacitor C is connected in shunt/parallel with load resistor (R_L)



Ripple Factor for Capacitor Filter of a Half Wave Rectifier is given by

Ripple Factor for a capacitor filter (HWR) = $1 / (2\sqrt{3} f C R_L)$

f – Frequency of AC input Signal

R_L – Value of Load resistor

C – Capacitance of the Shunt Capacitor

$$\gamma = \frac{V_{r(rms)}}{V_{dc}}, V_{r(rms)} = \frac{I_{DC}}{2\sqrt{3}fc},$$

$$V_{dc} = V_m - \frac{I_{DC}}{2fc}$$

1. A full wave rectifier with C filter is supplying a load of $500\ \Omega$. If the ripple factor should not exceed 10 %, find the value of capacitor required. Assume input AC signal frequency is 50 Hz. What is the new value of ripple if capacitor of $500\ \mu\text{F}$ is connected across the load?

Solution:

Given $\gamma = 10\ \% = 0.1$ and $R_L = 500\ \Omega$

$$\gamma = \frac{1}{4\sqrt{3} f C R_L}$$

$$C = \frac{1}{4\sqrt{3} f \gamma R_L} = \frac{1}{4\sqrt{3} \times 50 \times 0.1 \times 500} = 57.73\ \mu\text{F}$$

If a capacitor of $500\ \mu\text{F}$ is used the ripple factor is

$$\gamma = \frac{1}{4\sqrt{3} f C R_L} = \frac{1}{4\sqrt{3} \times 50 \times 500 \times 10^{-6} \times 500} = 0.0115$$

2. In a full wave rectifier with C filter the output DC voltage is 10 V and load current is 10 mA. Calculate the value of capacitance required such that the output DC voltage will have ripple ≤ 0.001 .

Solution:

$$R_L = \frac{V_{dc}}{I_{dc}} = \frac{10}{10 \text{ m}} = 1 \text{ K}\Omega$$

Assume frequency of input AC signal, $f = 50 \text{ Hz}$

$$\gamma = \frac{1}{4 \sqrt{3} f C R_L}$$

$$C = \frac{1}{4 \sqrt{3} f \gamma R_L} = \frac{1}{4 \sqrt{3} \times 50 \times 0.001 \times 1 \times 10^3} = 2886 \mu\text{F}$$

3. Calculate the RMS value of the ripple voltage for the FWR in a $100\mu\text{F}$ Capacitor connected to a load drawing 50mA of current .What is the dc voltage at the output if the peak rectified output voltage is 30V and frequency is 50Hz . Also find the ripple factor

Solution:

$$\gamma = \frac{V_{r(rms)}}{V_{dc}}, V_{r(rms)} = \frac{I_{DC}}{4\sqrt{3}fc},$$

$$V_{dc} = V_m - \frac{I_{DC}}{4fc}$$

Given :

$I_{dc} = 50\text{mA}$, $f = 50\text{Hz}$, $C = 100\mu\text{F}$

Therefore $V_{rms} = 1.4\text{V}$

$V_m = 30\text{V}$

Therefore $V_{dc} = 27.5\text{V}$

Ripple factor = 0.05

4. A Half wave rectifier with C filter is supplying a resistive load of 500Ω . If the load ripple content should not exceed 10% find the value of C required

Solution:

For a Half wave rectifier with C filter ,

$$\text{Ripple Factor} = \frac{1}{2\sqrt{3} f C R_L}$$

$$0.10 = \frac{1}{2\sqrt{3} * 50 * C * 500}$$

$$C = 0.115 \text{mF}$$

5. A $100\mu\text{F}$ capacitor when used as a filter has 15V rms across it with a load resistor of $2.5\text{K}\Omega$. If the filter is the full wave and supply frequency is 50Hz , what is the percentage of ripple factor in the output?

Solution:

For a full wave rectifier with C filter ,

Ripple factor, $\gamma = \frac{1}{4\sqrt{3}} f C R_L$

$$= \frac{1}{4\sqrt{3}} * 50 * 100 * 10^{-6} * 2.5 * 10^{-3}$$

$$= 0.01154.$$

So, ripple factor is 1.154%

6. A full wave rectifier uses a capacitor filter with $500\mu\text{F}$ capacitor and provides a load current of 200mA at 8% ripple. Calculate the dc voltage and the value of peak rectified voltage?

Solution:

The ripple factor for Full Wave Rectifier with C filter

$$r = \frac{1}{4\sqrt{3} f C R_L} \text{ substituting } R_L = V_{dc}/I_{dc}$$

$$\text{We know, } V_m = V_{dc} + I_{dc}/4fC$$

$$r = \frac{I_{dc}}{4\sqrt{3} f C V_{dc}}$$

$$= 14.43 + \{ 200 * 10^{-3} / \{ 4 * 50 * 500 * 10^{-6} \} \}$$

after re-arranging

$$= 14.43 + 2 = 16.43\text{V}$$

$$V_{DC} = 200 * 10^{-3} / 4\sqrt{3} * 50 * 500 * 10^{-6} * 0.08$$

$$V_m = 16.43\text{V}$$

$$V_{DC} = 14.43\text{V}$$



THANK YOU

Department of Electronics and Communication